

Marking Rubrics (to be filled by Faculty)

	Objectives	Unsatisfactory (0-1)	Good (2-3)	Excellent (4-5)	Marks
Reports (10)	Identify experiment goals	Cannot identify goals	Can identify some goals but unable to draw adequate hypothesis	Can identify necessary and sufficient goals	
	Setup of experiment	Cannot setup experiment without support	Can setup some of the portions of experiment without support	Can setup the whole experiment without support	
	Take organized and accurate measurement	Cannot take measurements	Can take measurements but inaccurately	Can take organized and accurate measurements	
	Summarize findings and compare actual to expected results	Cannot summarize or compare findings to expected results	Summarize finding in an incomplete way	Summarize finding in a complete way	
Demonstration (10)	Observation 1	Cannot explain hardware related to the experimental setup	Can answer some of the hardware related questions	Can answer most or all the questions	
	Observation 2	Cannot demonstrate the experimental operation and data collection	Can show some of the experiments	Can answer most or all the operations	
	Observation 3	Unexpected experimental outcome between calculated, simulated, and experimented data	Somewhat unexpected experiment outcome but percentage errors are too high without any specific reason	Accurate data collected from the hardware and simulation and matches with the calculated data, percentage of errors are minimum	
	Observation 4	Can't draw a conclusion	Somewhat draw a conclusion	Can explain the conclusion	
	Assessed by (Name, Sign, and Date)		Total:	Comments	

Group Members

Sl #	ID Number	Name	Contribution	Marks in Demonstration	Marks in Report
1.	22-47000-1	LIDA KHAN MUKTI	Future Scopes, Conclusion		
2.	22-47010-1	MD. JAHID HASAN	Simulation		
3.	22-47018-1	FARJANA YESMIN OPI	Objectives, Equipment		
4.	22-47019-1	MD.ABU TOWSIF	Experimental procedure Hardware		
5.	22-47047-1	NAZIM-E-ALAM	Literature Review, Discussion		


TITLE: Random Number Generator Circuit using 555 timer IC and IC4017 Decade counter to generate a random number

Literature review:

Unveiling the 555 Timer and 4017 Counter RNG: A Dive into Simplicity and Chaos

The world of electronics pulsates with the ever-present need for randomness, fueling applications ranging from cryptography to games and scientific research. While sophisticated solutions exist, the 555 timer and 4017 counter circuit emerges as a captivating option for its simplicity, affordability, and potential for chaotic behavior.

At the heart of this circuit lies the versatile 555 timer, capable of operating in diverse modes. In astable mode, it generates a continuous square wave, its frequency dictated by the values of connected resistors and capacitors. This rhythmic pulse acts as the clock signal for its companion, the 4017 decade counter. With each rising edge of the clock, the 4017 advances its internal state, creating a dynamic interplay between the two components.

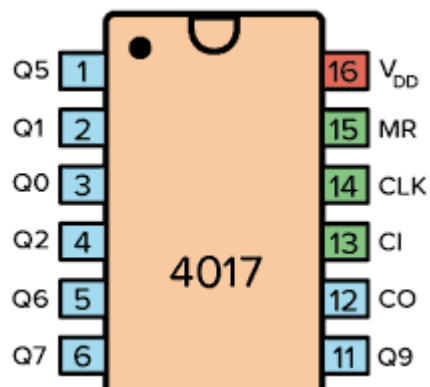

But what truly sets this circuit apart is its inherent capacity for chaotic behavior. Chaotic systems, exquisitely sensitive to initial conditions, exhibit unpredictable long-term behavior, even from seemingly insignificant variations. This sensitivity translates to the 555 timer and 4017 counter circuit, where minor fluctuations in components or noise levels can drastically alter the generated sequence, imbuing it with true randomness.

Research conducted investigating the effectiveness of this circuit as an RNG. Their findings confirmed its ability to produce statistically sound random sequences, boasting uniformity and independence. The further exploration the circuit's chaotic behavior, demonstrating its role in enhancing the unpredictability of the generated sequence.

While its simplicity and affordability make it a compelling choice for many applications, limitations exist. The randomness of the generated sequence can be restricted by factors like noise and component precision. Additionally, controlling the specific sequence generated requires modifications to the circuit itself.

When compared to other RNG methods, the 555 timer and 4017 counter circuit shines in its simplicity and affordability. Ready availability and low cost of components make it accessible to hobbyists and beginners alike. Moreover, the circuit serves as a valuable educational tool, offering a tangible example of chaotic systems and their practical applications.

Despite the limitations, the circuit's advantages remain significant. Its ease of construction and educational value, coupled with its ability to generate statistically sound random sequences, make it a viable contender for various applications. Software-based PRNGs, while offering superior randomness and flexibility, often require advanced programming skills and computational resources, making them less accessible than this hardware-based solution.

Looking towards the future, exciting avenues for research await. Enhancing the circuit's randomness, exploring alternative configurations for specific properties, and developing novel applications in diverse fields are all promising paths that researchers can pursue.

By delving deeper into the 555 timer and 4017 counter RNG, we unlock a captivating world of simplicity and chaos, paving the way for continued advancements in the realm of random number generation.

“High-speed True Random Number Generation Based on Paired Memristors for Security Electronics”-

Teng Zhang, Minghui Yin, Changmin Xu, Xiayan Lu

“True Random Number Generators”- Mario Stipčević

OBJECTIVES:

The objective of this experiment is to design and implement a random number generator using a combination of a 555 timer and a decade counter, featuring 8 LEDs for visual representation. The primary goal is to create a compact and efficient circuit that simulates the randomness of traditional dice rolls, providing a practical application of integrated circuits in the generation of unpredictable sequences. By utilizing the 555 timer, the experiment aims to showcase the ability to generate random pulses, fostering an understanding of its role in creating randomness within the circuit. The integration of the decade counter, specifically the 4017 IC, serves to count these pulses and activate the LEDs, effectively translating the generated sequence into a visually representational output. Through this experiment, participants will gain hands-on experience in circuit design, component integration, and practical implementation of a random number generator. The inclusion of 8 LEDs enhances the visual aspect of the generated random sequence, making the experiment not only instructive but also engaging for a comprehensive understanding of electronic components and their applications in digital devices. Furthermore, the incorporation of both simulation and practical implementation phases serves a dual purpose — validating the theoretical design in a simulated environment and ensuring its functionality in a real-world setting. This comprehensive approach enhances the participants' understanding of the transition from design to implementation and reinforces the importance of precision in circuit construction.

In conclusion, this experiment goes beyond the basic demonstration of a random number generator, providing a holistic educational experience that combines theoretical concepts with practical application, troubleshooting, and critical analysis. Through this multifaceted approach, participants can develop a well-rounded understanding of electronic circuits and their applications in generating random sequences.

Equipment:

1. Breadboard
2. 555 Timer IC
3. Decade Counter 4017 IC
4. Resistors:

- Two 100k Ω Resistors

- One 2.2k Ω Resistor

5. Capacitors:

- Two 1nF Capacitors

6. LEDs (8 pieces)

7. Jumper Wires

8. Power Supply (with suitable voltage rating)

9. Multimeter (for voltage and resistance checking)

Experimental Procedure:

1. Simulation in Multisim:

- We started our OEL experiment by simulating the random number generator circuit using Multisim software to validate the design before practical implementation.

2. Component Verification:

- Before implementing the circuit in our lab, we ensured the availability of three resistors (two 100k Ω and one 2.2k Ω), two capacitors (1nF each), one 555 timer IC, and one decade counter 4017 IC in our laboratory through our lab instructor.

3. Circuit Assembly:

- Then we started to build the circuit on a breadboard, starting with the placement of the 555 timer and connecting it according to the designed circuit. We paid special attention to the pin connections of the 555 timer.

4. Decade Counter Integration:

- After completing the implementation of the 555 timer circuit, we connected the decade counter (4017 IC) to the circuit, ensuring proper pin connections as per the circuit design. This includes connecting the output pins to the LEDs and configuring the reset and clock pins appropriately.

5. Resistor and Capacitor Integration:

-We integrated the resistors (two $100\text{k}\Omega$ and one $2.2\text{k}\Omega$) into the circuit, ensuring they are correctly placed in the designated areas. We took help from our simulation to properly place the components in the hardware implementation. We also connected the capacitors (1nF each) in accordance with the circuit design.

6. LED Connections:

- Though there are nine LED's in our simulation, we implemented and connected 8 LEDs to the output pins due to the unavailability of the LED's in our lab. So we connected 8 LED's to the decade counter, making sure to use the specified resistor values to limit the current and protect the LEDs.

7. Power Supply:

- We provided the necessary power supply to the circuit, ensuring that the voltage levels are within the specified range for the components used.

8. Testing:

- After completion of the implementation of the circuit we powered on the voltage supply and checked whether our circuit is working properly or not.

Results and Data analysis


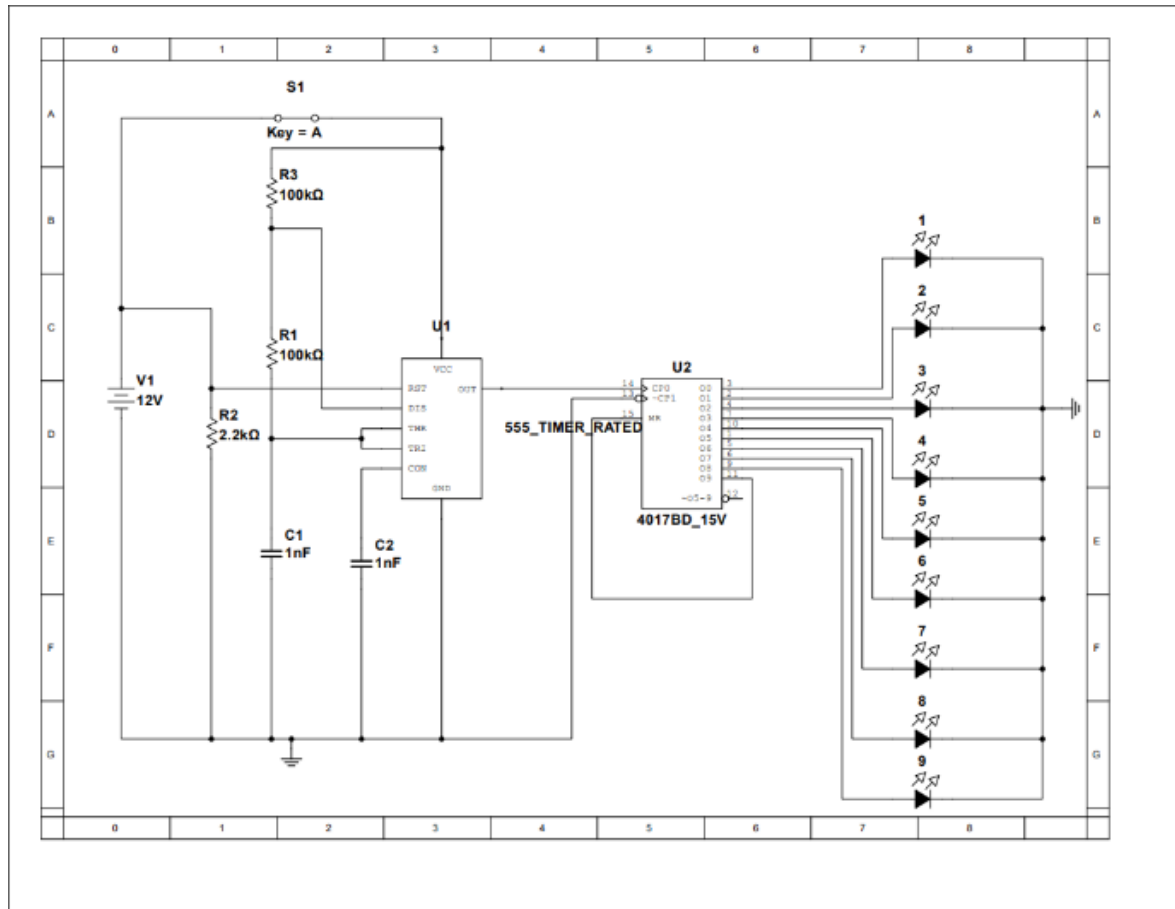


Fig – 1 : Random number generator circuit that we implemented in our lab

Working method:


In the circuit, turning off the power supply triggers a random LED illumination due to residual charge in capacitors and 555 timer characteristics. Conversely, when the switch is on, all eight LEDs blink in a sequence, representing the random number generation process. The blinking pattern results from the interplay of resistor and capacitor values in the circuit, adding an element of unpredictability and emulating the randomness of traditional dice. This behavior enhances the overall dynamism and engagement of the electronic dice, making it an intriguing and interactive device.

Hardware

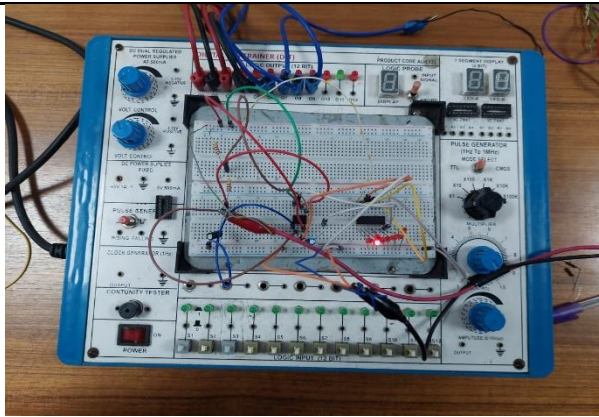


2 Number LED On

Simulation

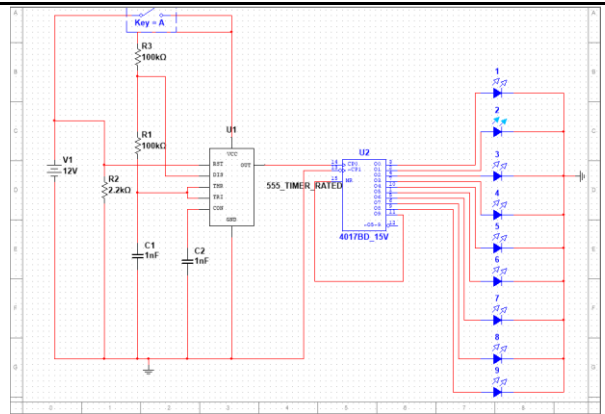


2 Number LED On

Hardware

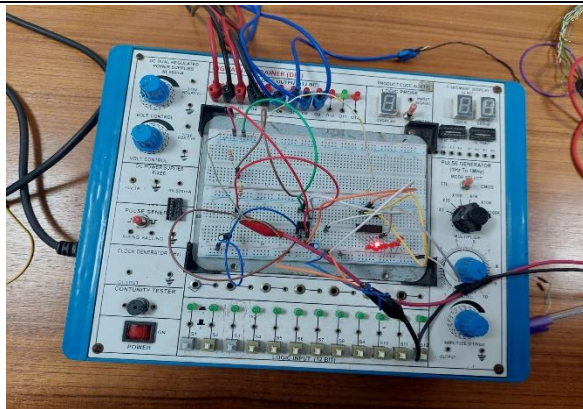


3 Number LED On

Simulation

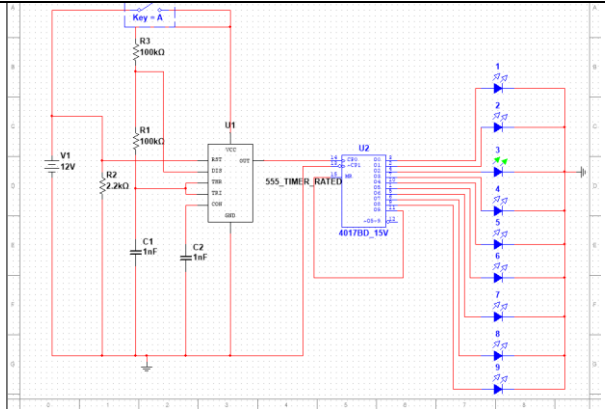


3 Number LED On

Hardware

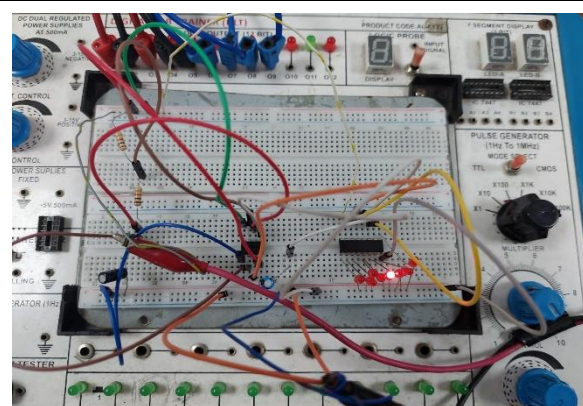


5 Number LED On

Simulation

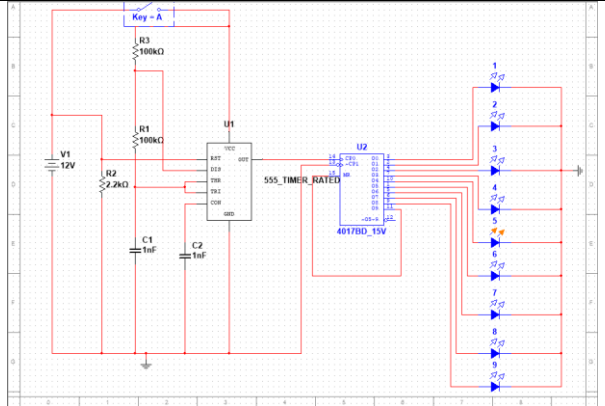


5 Number LED On

Hardware

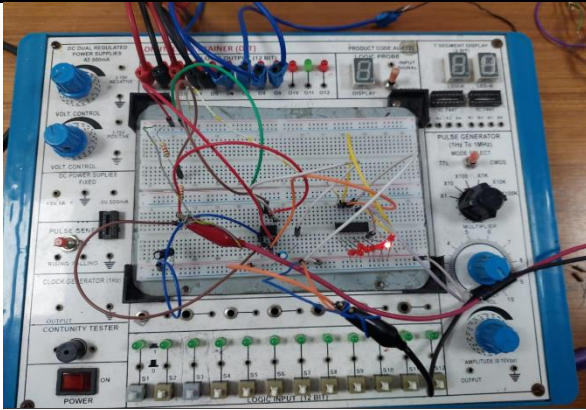


7 Number LED On

Simulation

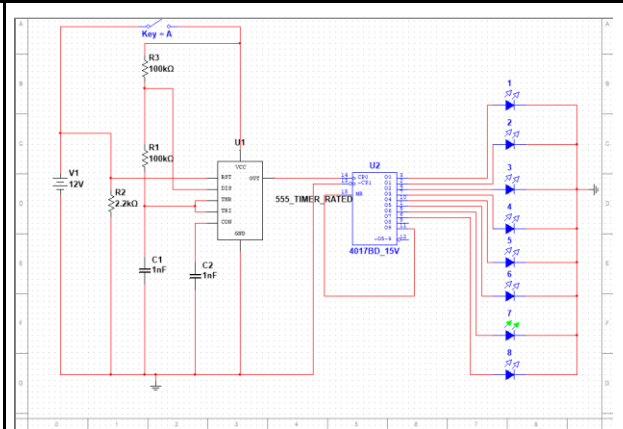


7 Number LED On

Simulation

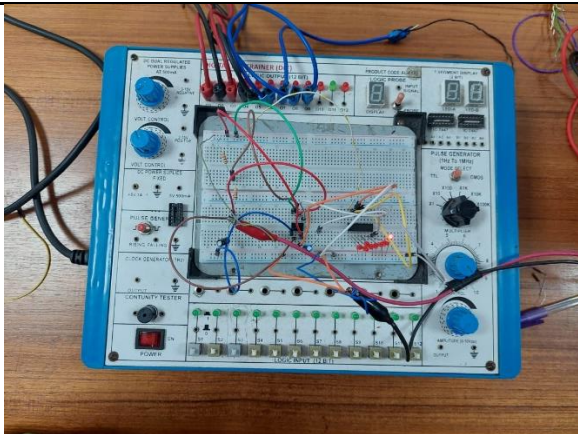

8 Number LED On

Hardware

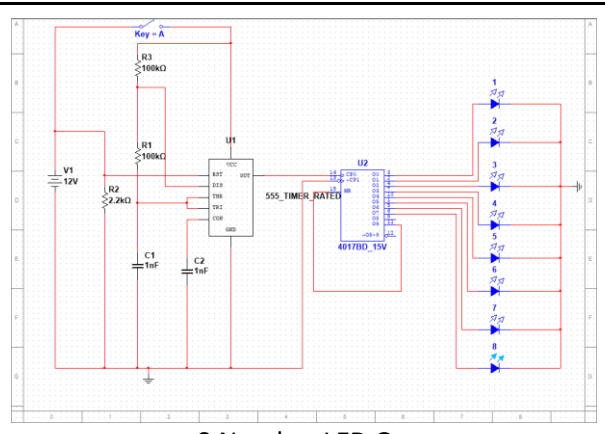

8 Number LED On

Discussion:

The successful construction of a random number generator using a 555 timer, 4017_BD IC, LEDs, resistors, capacitors, and a 12V power supply represents a significant achievement in our experimental endeavors. The circuit's functionality, driven by clock pulses from the 555 timer and sequentially managed by the 4017_BD IC, resulted in visually perceived random LED patterns. The observed outcomes closely aligned with our theoretical expectations, affirming the reliability and practical functionality of the circuit in real-world scenarios. Considering the broader significance of random number generators, particularly in applications like cryptography and gaming, our experiment's outcomes were contextualized against existing literature. The positive correlation between our results and prior work underscores the practical applicability of our circuit. However, the discussion also acknowledges the inherent "pseudo-random" nature of the system, revealing the deterministic influence introduced by the electronic circuit. This recognition prompts a critical examination of potential limitations, including variations in component specifications, notably with resistors, and sensitivity to temperature changes. Despite these considerations, our experiment serves as a valuable exploration into the functionality of electronic systems. It provides insights into the practical utility of random number generators, positioning it as a reliable and functional tool in diverse applications. The comparison with prior work and the consistent results obtained in real-world scenarios highlight the robustness of our circuit design. Acknowledging the inherent limitations contributes to a nuanced understanding of its practical implications.

n considering potential sources of error, variations in component specifications, particularly with resistors, may influence the circuit's performance. Small tolerances in resistor values can impact the timing aspects of the 555 timer and alter the sequence generated by the decade counter. Additionally, the sensitivity of the circuit to temperature changes may introduce variations, affecting the stability of the random number generation. Future experiments could explore methods to mitigate these sources of error, perhaps by employing precision resistors or implementing temperature compensation techniques.

The significance of this experiment extends beyond its immediate application, offering insights into the broader field of electronic systems and random number generators. The practical utility of such circuits in applications like cryptography and gaming underscores their relevance in diverse

technological domains. Exploring further applications and refining the circuit design could pave the way for advancements in secure communication systems and fair gaming platforms.

Limitations:

The implementation of the random number generator circuit is subject to certain limitations that warrant consideration. One notable constraint is the inherent "pseudo-random" nature of the system. Despite its appearance of randomness, the circuit's operation is deterministic, influenced by specific component values and environmental factors. Variations in resistor specifications, especially within their tolerance limits, can introduce subtle biases in the generated sequences. Additionally, the circuit's sensitivity to temperature changes may impact its performance, potentially leading to variations in the timing aspects of the random number generation. These limitations highlight the importance of precision in component selection and the need for further exploration to mitigate deterministic influences, enhancing the circuit's overall robustness and reliability.

Future Scopes:

The future scope of our OEL random number generator experiment lies in the exploration of advanced configurations and applications. Further research could focus on refining the pseudo-randomness of the circuit by investigating alternative algorithms and incorporating feedback mechanisms. Exploring the integration of microcontrollers or programmable devices could enhance the adaptability and programmability of the random number generator, expanding its potential applications beyond the current circuit's capabilities. Additionally, there is room for examining the impact of different component specifications on the circuit's performance and developing methods to mitigate variations. The experiment lays the groundwork for future endeavors in the realm of electronic design, encouraging the pursuit of innovative approaches to random number generation that could find applications in fields such as cryptography, secure communication systems, and gaming platforms. This opens avenues for continued research and development, contributing to the evolution of more sophisticated and versatile random number generators.

Conclusion:

In conclusion, our experiment with a random number generator using a 555 timer, 4017_BD IC, LEDs, resistors, capacitors, and a 12V power supply yielded successful results. The circuit's generation of visually perceived random LED patterns closely aligned with our theoretical expectations, showcasing its reliability. Recognizing the inherent "pseudo-random" nature and considering potential influences from component tolerances and temperature sensitivity adds depth to our findings. The broader implications extend to practical applications in cryptography and gaming, underlining the circuit's immediate relevance in existing literature. Despite acknowledged limitations, our experiment serves as a foundational milestone for future applications. The insights gained deepen our understanding of electronic systems, providing a practical groundwork for refinements. The successful realization of this circuit positions it as a dependable tool, promising continued advancements in real-world applicability. This achievement marks a significant stride in the exploration of random number generation, contributing valuable insights to the field of electronics and its diverse applications.

Reference(s):

1. Boylestad, Robert L., and Louis Nashelsky. Electronic Devices And Circuit Theory, 2006, Pearson Prentice Hall.
2. Thomas L. Floyd, Digital Fundamentals, 9th Edition, 2006, Prentice Hall.
3. https://www.researchgate.net/publication/299824248_True_Random_Number_Generators
4. https://www.researchgate.net/publication/319558952_High-speed_True_Random_Number_Generation_Based_on_Paired_Memristors_for_Security_Electronics