

Lecture -1

Logic Gates & Boolean Algebra

Prepared By: Asif Mahfuz



Logic Gates

- Logic Gates are the basic building blocks of any digital system.
- A logic gate can have one or more than one input but only one output.
- The relationship between the input/s and the output is based on a certain logic.
- The gates are named based on the logic.

Basic Logic Gates

- NOT gate
- AND gate
- OR gate

Universal Logic Gates

- NAND gate
- NOR gate

Exclusive Logic Gates

- XOR gate
- XNOR gate


NOT Gate (Inverter)

- The output an inverter (NOT gate) is the opposite of its input.

Inverter truth table.




Input	Output
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)

$X = \overline{X}$

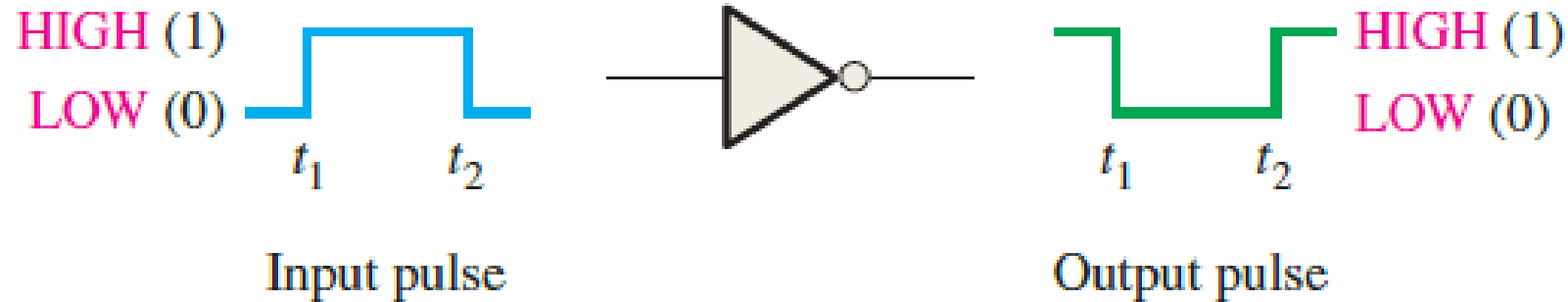

AND Gate

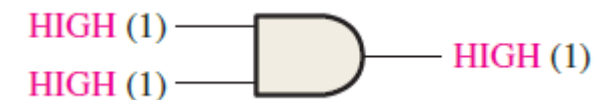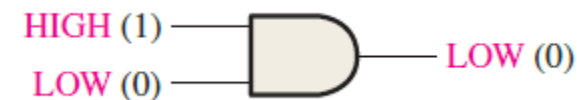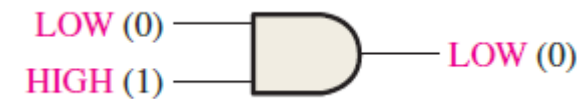- The output an AND gate is **HIGH** only when both the inputs are **HIGH**.



Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1


HIGH = On
LOW = Off

HIGH = Unbuckled
LOW = Buckled

Ignition switch *A*


Seat belt *B*

$$X = AB$$

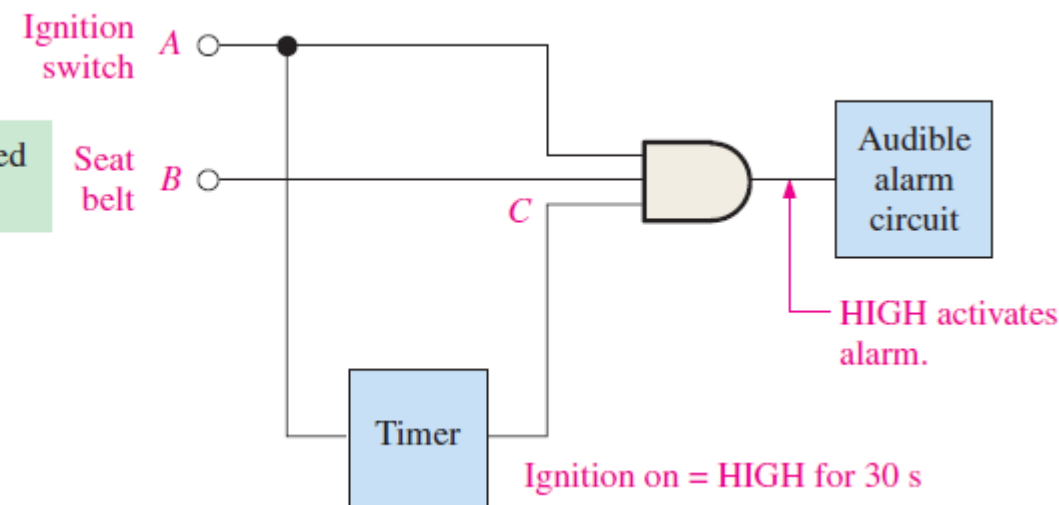

OR Gate

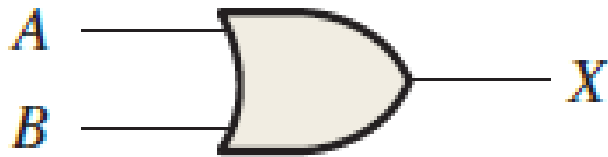- The output an OR gate is HIGH when anyone or both the inputs are HIGH.



LOW (0) — LOW (0) — LOW (0)

HIGH (1) — HIGH (1)

LOW (0) — HIGH (1)


HIGH (1) — HIGH (1)

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

$$X = A + B$$






Open door/window sensors

HIGH = Open
LOW = Closed

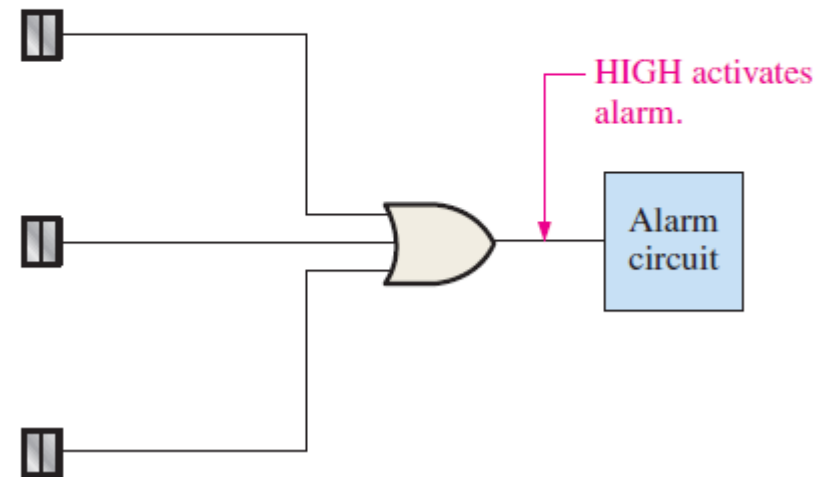

NAND Gate

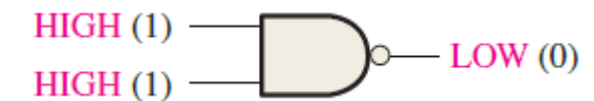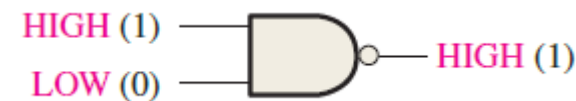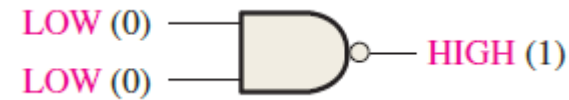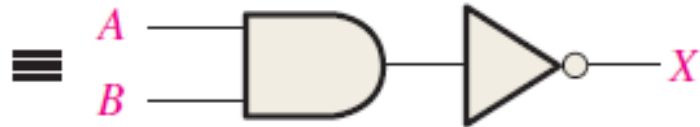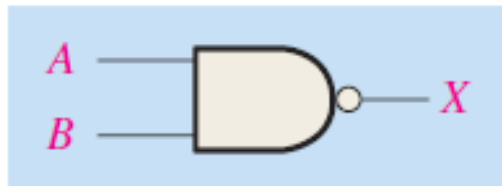- The output of a NAND gate is **HIGH** whenever one or more inputs are **LOW**.



NAND


Negative-OR

Inputs

Output


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

$$X = \overline{AB}$$

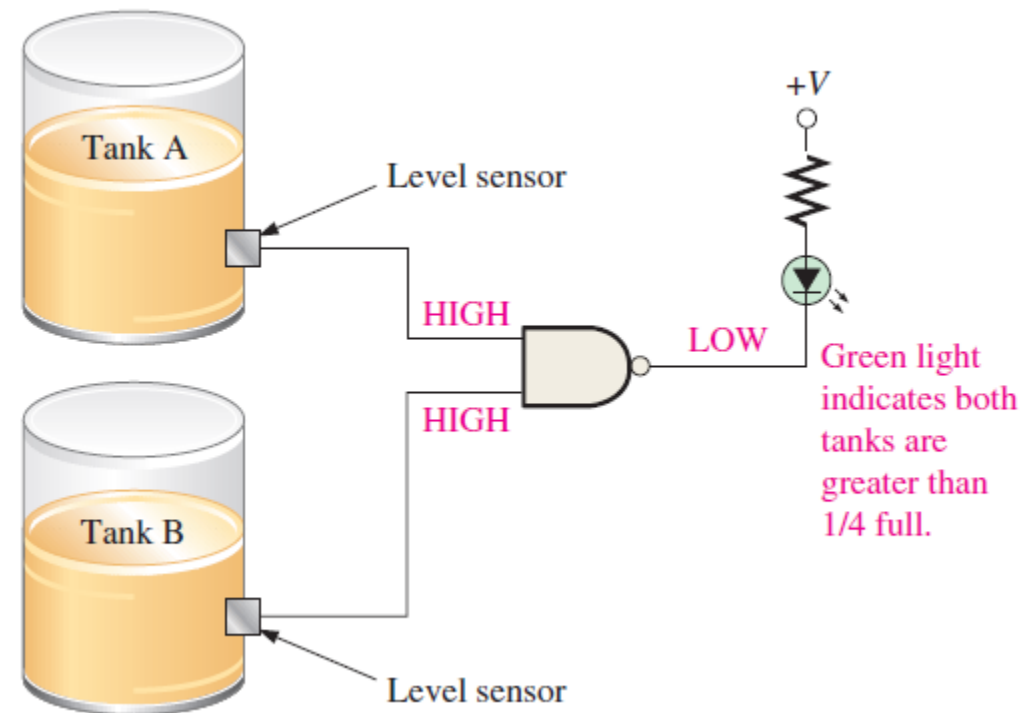

NOR Gate

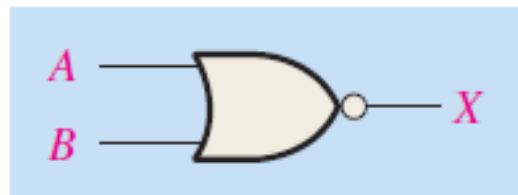- The output of a NOR gate is **LOW** whenever one or more inputs are **HIGH**.




NOR

Negative-AND

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

$$X = \overline{A+B}$$

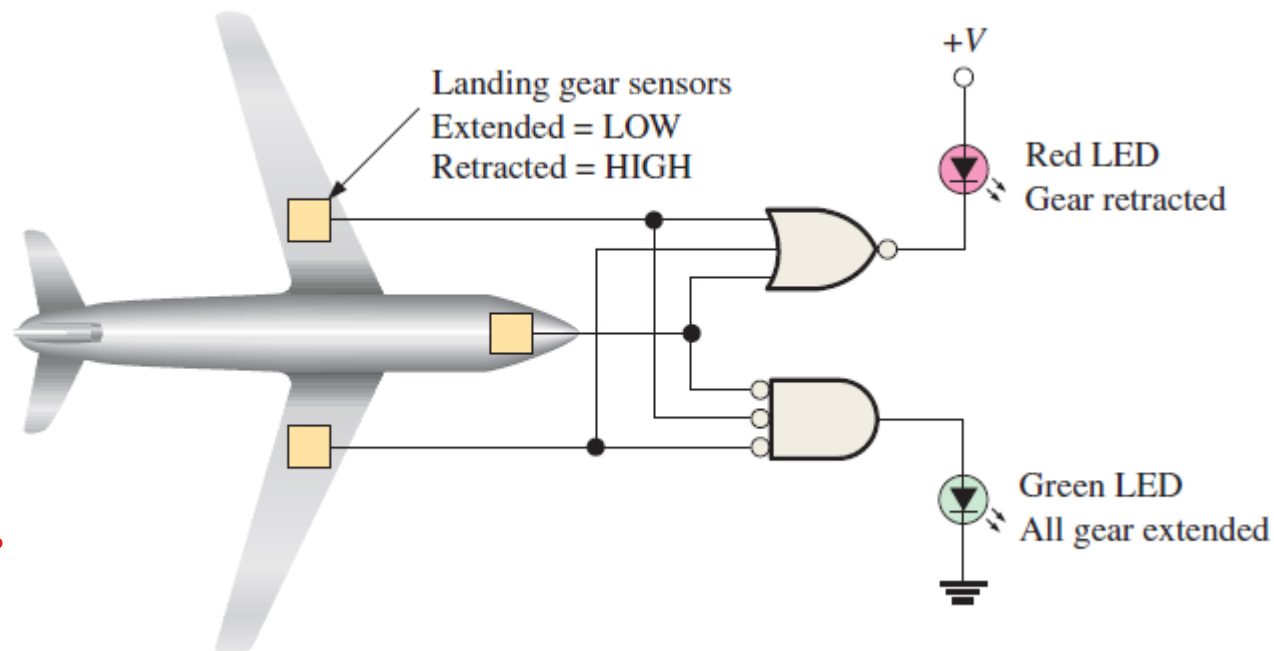

XOR Gate

- The output of a XOR gate is **HIGH** whenever the two inputs are different.




Truth table for an exclusive-OR gate.

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0


$$X = A \oplus B$$

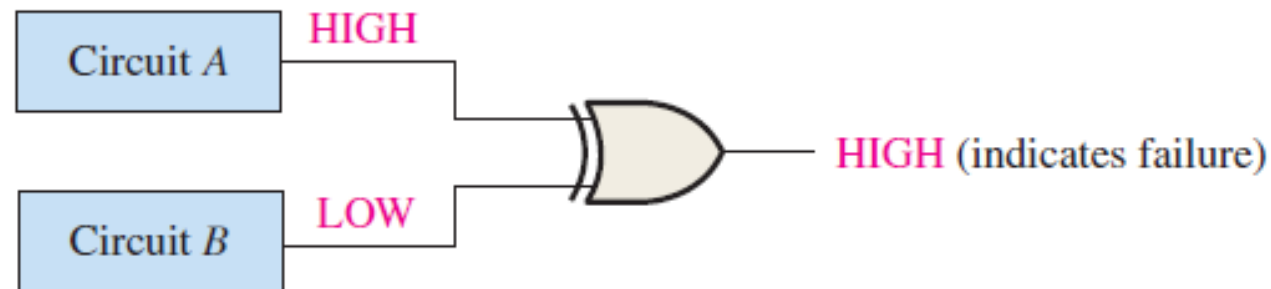Two circuits are supposed to work parallelly in a process. If any of the circuit fails an indicator is activated.



XNOR Gate

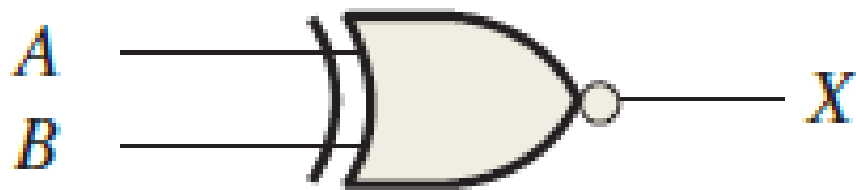- The output of a XNOR gate is gate is HIGH whenever the two inputs are same.



LOW (0) — HIGH (1)
LOW (0) —



LOW (0) — LOW (0)
HIGH (1) —



HIGH (1) — LOW (0)
LOW (0) —



HIGH (1) — HIGH (1)
HIGH (1) —





Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

$$X = \overline{A \oplus B}$$

Boolean Algebra

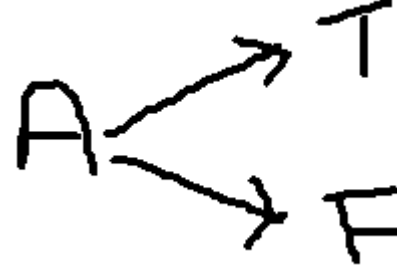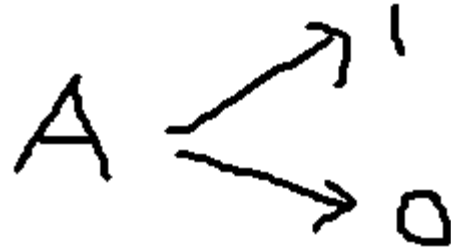- Boolean Variable: These are variables which can either take the value 1 or 0.



- Boolean Logic Expression: A Boolean logic expression is an expression constituted of only Boolean variables. The output of a Boolean logic expression is a Boolean value i.e. either True/False.


$$AB + A(B + C) + B(B + C)$$

- Boolean Algebra: It is the mathematics of digital logic. Usually Boolean algebra is used to simplify Boolean expressions or Boolean Function.


Laws of Boolean Algebra

Commutative Law:

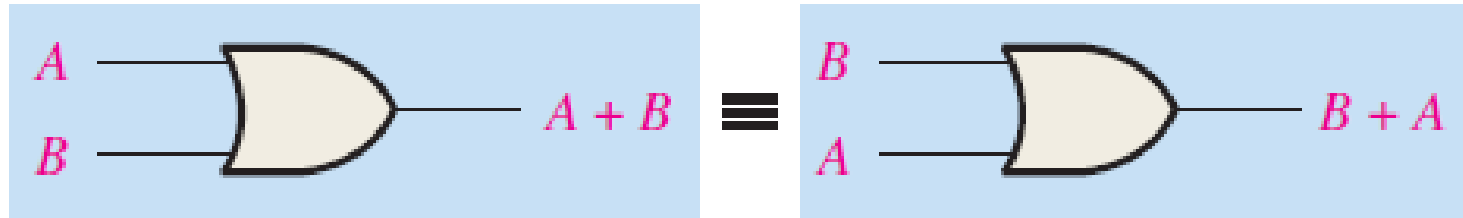- The commutative law for addition can be written as $A+B=B+A$



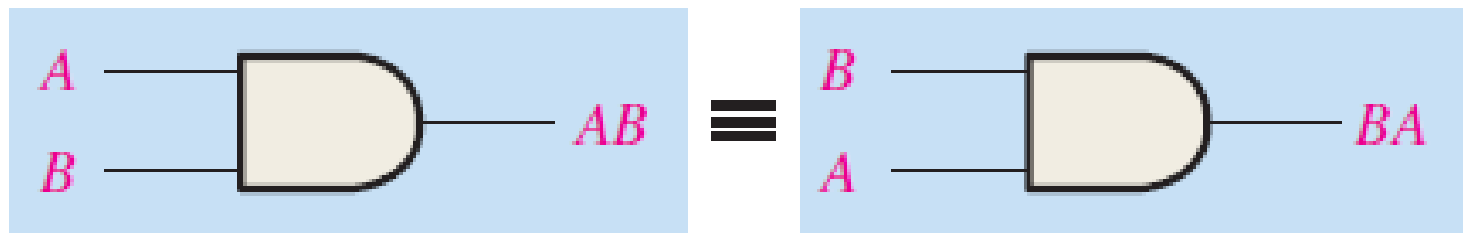
- The commutative law for multiplication can be written as $AB=BA$




Laws of Boolean Algebra

Associative Law:

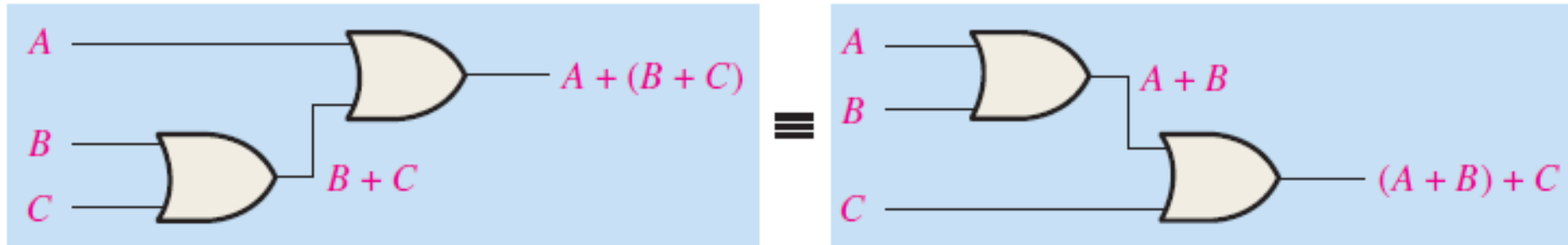- The associative law of addition for three variables is written as $A + (B + C) = (A + B) + C$



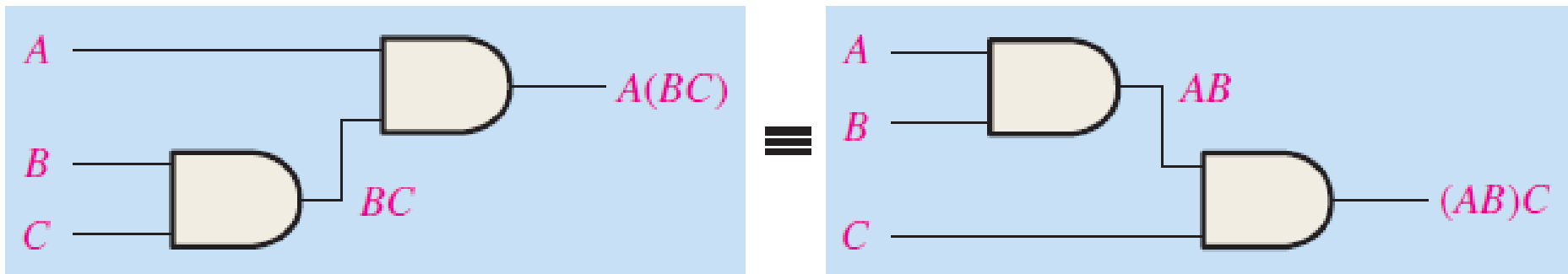
- The associative law of multiplication for three variables is written as $A(BC) = (AB)C$



Laws of Boolean Algebra


Distributive Law:

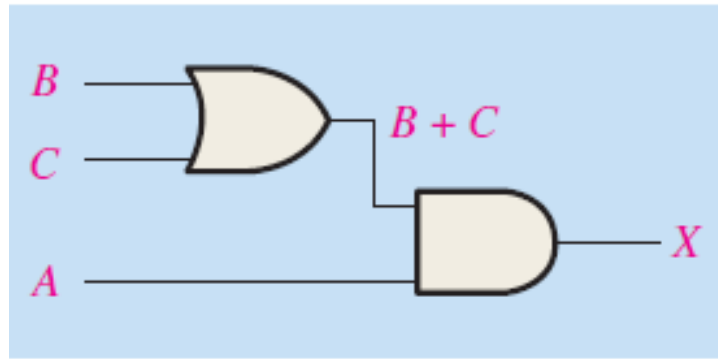- The distributive law for three variables is written as $A(B+C)=AB+AC$



$$X = A(B + C)$$

\equiv

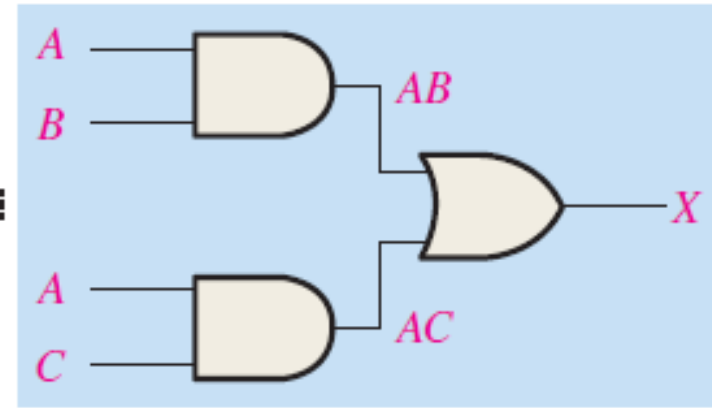

$$X = AB + AC$$

Basic rules of Boolean algebra.

1. $A + 0 = A$

2. $A + 1 = 1$

3. $A \cdot 0 = 0$

4. $A \cdot 1 = A$

5. $A + A = A$

6. $A + \bar{A} = 1$

7. $A \cdot A = A$

8. $A \cdot \bar{A} = 0$

9. $\overline{\bar{A}} = A$

10. $A + AB = A$

11. $A + \bar{A}B = A + B$


12. $(A + B)(A + C) = A + BC$

De Morgan's Theorem

The first theorem is stated as follows:

- The complement of a product of variables is equal to the sum of the complements of complements of the variable.
- The formula of this theorem for two variables is written as:

$$\overline{XY} = \bar{X} + \bar{Y}$$

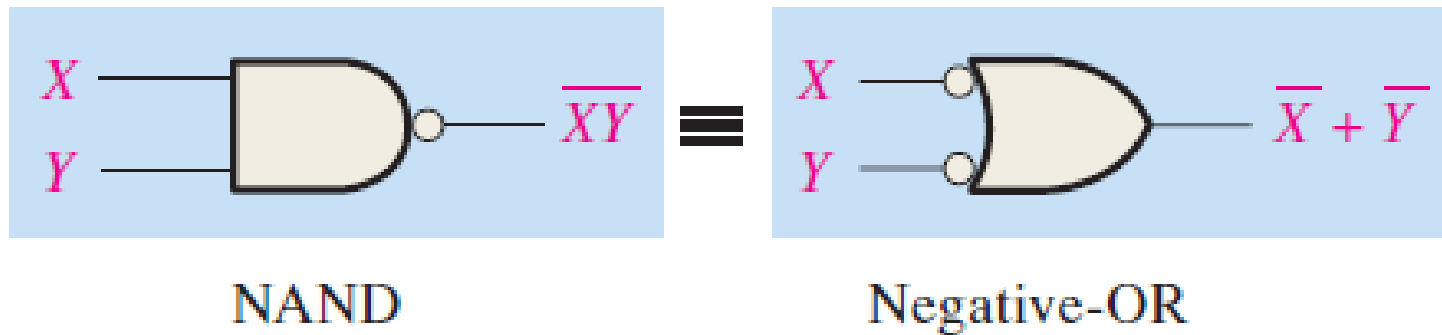


Inputs		Output	
X	Y	\overline{XY}	$\bar{X} + \bar{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

De Morgan's Theorem

The second theorem is stated as follows:

- The complement of a sum of variables is equal to the product of the complements of the variables.
- The formula of this theorem for two variables is written as:
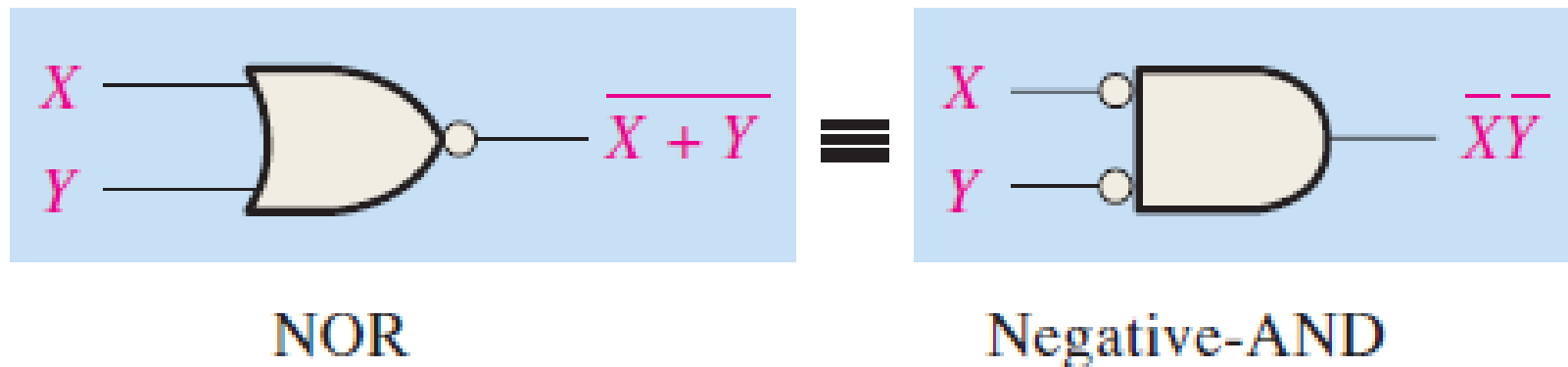
$$\overline{X + Y} = \bar{X} \cdot \bar{Y}$$



Inputs		Output	
X	Y	$\overline{X + Y}$	$\bar{\bar{X}} \bar{\bar{Y}}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Application of De Morgan's Theorem

Apply DeMorgan's theorems to the expressions \overline{XYZ} and $\overline{X + Y + Z}$.

Solution

$$\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{X + Y + Z} = \overline{X} \overline{Y} \overline{Z}$$

Apply DeMorgan's theorems to the expressions \overline{WXYZ} and $\overline{W + X + Y + Z}$.

Solution

$$\overline{WXYZ} = \overline{W} + \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{W + X + Y + Z} = \overline{W} \overline{X} \overline{Y} \overline{Z}$$

Apply DeMorgan's theorems to each expression:

(a) $\overline{(\overline{A} + \overline{B}) + \overline{C}}$

(b) $\overline{(\overline{A} + B) + CD}$

(c) $\overline{(A + B)\overline{C}\overline{D} + E + \overline{F}}$

Solution

(a) $\overline{(\overline{A} + \overline{B}) + \overline{C}} = \overline{(\overline{A} + \overline{B})} \overline{\overline{C}} = (A + B)C$

(b) $\overline{(\overline{A} + B) + CD} = \overline{(\overline{A} + B)} \overline{CD} = (\overline{\overline{A}B})(\overline{C} + \overline{D}) = A\overline{B}(\overline{C} + \overline{D})$

(c) $\overline{(A + B)\overline{C}\overline{D} + E + \overline{F}} = \overline{((A + B)\overline{C}\overline{D})} \overline{(E + \overline{F})} = (\overline{A}\overline{B} + C + D)\overline{E}F$

Application of De Morgan's Theorem

Apply DeMorgan's theorem to the expression $\overline{\overline{X} + \overline{Y} + \overline{Z}}$.

Apply DeMorgan's theorem to the expression $\overline{\overline{W}\overline{X}\overline{Y}\overline{Z}}$.

Apply DeMorgan's theorems to each of the following expressions:

(a) $\overline{(A + B + C)D}$

(b) $\overline{ABC + DEF}$

(c) $\overline{A\overline{B} + \overline{C}D + EF}$

The Boolean expression for an exclusive-OR gate is $A\overline{B} + \overline{A}B$. With this as a starting point, use DeMorgan's theorems and any other rules or laws that are applicable to develop an expression for the exclusive-NOR gate.

Starting with the expression for a 4-input NAND gate, use DeMorgan's theorems to develop an expression for a 4-input negative-OR gate.

Apply DeMorgan's theorems to the following expressions:


(a) $\overline{ABC} + (\overline{\overline{D} + E})$ (b) $\overline{(A + B)C}$ (c) $\overline{A + B + C} + \overline{\overline{D}E}$

Boolean Analysis of Logic Circuit

Boolean algebra provides a concise way to express the operation of a logic circuit formed by a combination of logic gates so that the output can be determined for various combinations of input values.

- A logic circuit can be expressed by Boolean expression and Boolean expression can be implemented by a logic circuit.
- The following Boolean expression can be implemented by the logic circuit below:

$$A(B + CD)$$

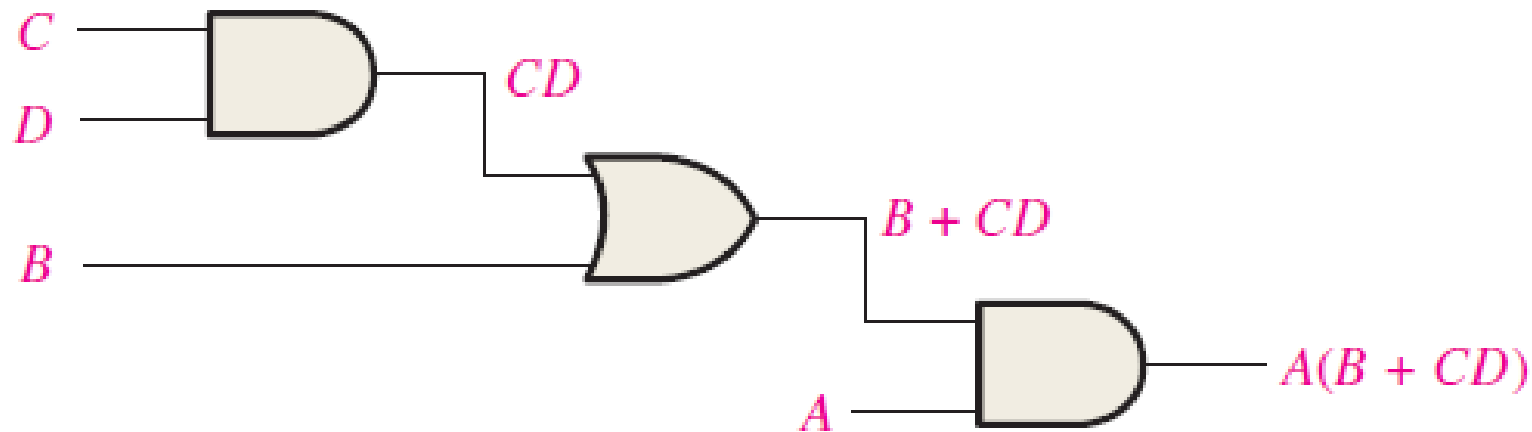

Constructing a Truth-table from a Boolean Expression

- Once we have the Boolean expression describing a process or a logical circuit, a truth-table to show the operation for all possible combination can be constructed.
- First, we need to determine the number of inputs in the expression.
- Then, we need to note down all possible combination of the inputs.
- Lastly, we will evaluation the expression for all possible combination.

$$A(B + CD)$$

Inputs				Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1



Logic Simplification

- We know that a Boolean expression can be implemented by a logical circuit.
- A large Boolean expression can often be simplified to a simpler and shorter expression.
- This is done by applying the laws and rules of Boolean algebra.
- Simplifying makes implementation simpler and thus requires lesser number of gates.
- Boolean algebra can be used to simplify the following expression:

$$AB + A(B + C) + B(B + C)$$

- The simplified expression is:

$$B + AC$$

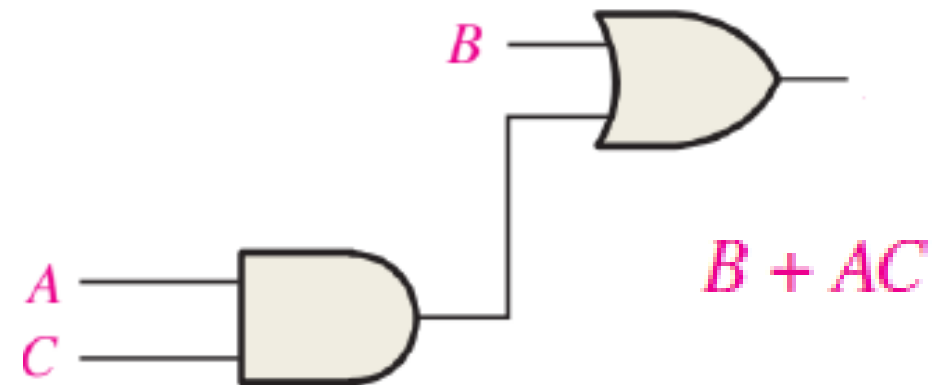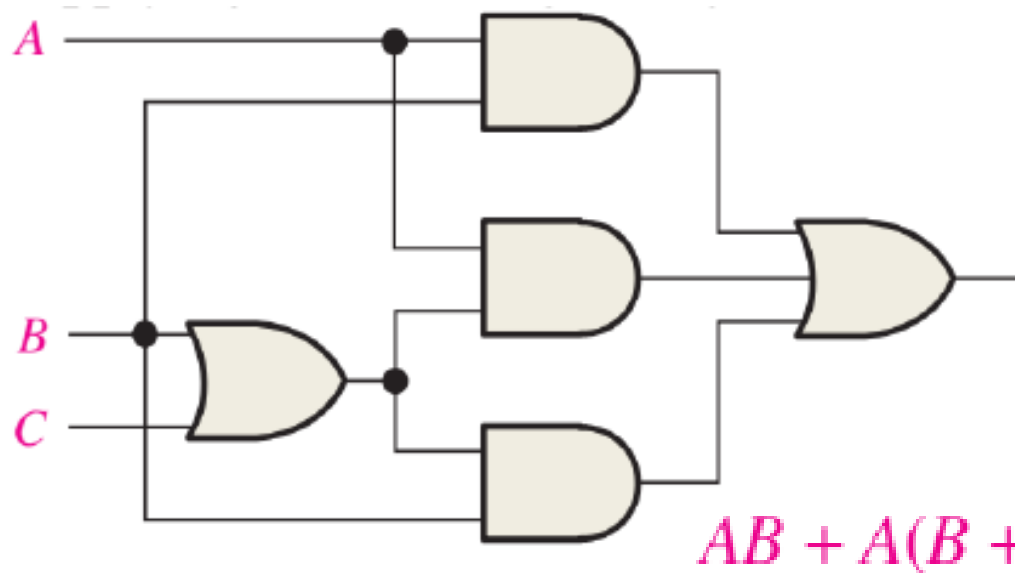

Logic Simplification

Simplify the Boolean expression $A\bar{B} + A(\overline{B + C}) + B(\overline{B + C})$.

Simplify the following Boolean expression:

$$[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$$

Simplify the following Boolean expression:

$$\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$$

Simplify the following Boolean expression:

$$\overline{AB + AC} + \bar{A}\bar{B}C$$

Simplify the Boolean expression $\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{A}\bar{B}\bar{C}$.

***Applying rules of Boolean algebra and DeMorgan's Theorem show that:

$$\text{i) } MN + \overline{M\bar{O}} + M\bar{N}O(MN + 0) = 1$$

$$\text{ii) } \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C = B$$

1. Simplify the following Boolean expressions:

$$\text{(a) } A + AB + A\bar{B}C \quad \text{(b) } (\bar{A} + B)C + ABC \quad \text{(c) } A\bar{B}C(BD + CDE) + A\bar{C}$$

2. Implement each expression in Question 1 as originally stated with the appropriate logic gates. Then implement the simplified expression, and compare the number of gates.

1. Thomas L. Floyd, “Digital Fundamentals” 11th edition, Prentice Hall – Pearson Education.

Thank You

Lecture -2

Sum-of-Products, Product-of-Sum

Prepared By: Asif Mahfuz



Standardization

- All Boolean expression, regardless of their form, can be converted into either of the two standard forms.
- The two standard forms are: Sum-of-Products (SOP) and Product-of-Sum (POS).
- Standardization makes evaluation, simplification and implementation of Boolean expression much more systematic and easier.

Domain of a Boolean Expression

- The domain of a general Boolean expression is the set of variable contained in the Boolean expression in either complemented or uncomplemented form.
- For example, the domain of the expression $A\bar{B} + \bar{A}C$ is the set of variable A,B and C.
- And for example, the domain of the expression $A\bar{B}C + \bar{C}E + \bar{A}\bar{D}$ is the set of variables A,B,C,D and E.

Sum-of-Product (SOP)

- Sum of Products: A Product is defined as a term consisting of products of the literals. When two or more products are summed in a Boolean expression, it is called the Sum-of-Products (SOP).

$$A + \bar{A}B + B\bar{C}$$

- Standard SOP: It is an expression where all the variables are present in each product terms. The products in a SSOP are called min terms (m_i).

$$ABC + \bar{A}BC + A\bar{B}C$$

- Conversion of SOP to Standard SOP
 - Step1: Multiply each of the non-standard terms with a term made up of the sum of the missing variable and its complement. This do not change the function as we are just multiplying by 1.
 - Step2: Repeat step 1 until all the non-standard terms become standard terms.

Sum-of-Products is used to describe when the function is 1.

Product-of-Sum (POS)

- Product of Sum: A Sum is defined as a term consisting of sum of the literals. When two or more sum terms are multiplied in a Boolean Expression, it is called the Product-of-Sum (POS).

$$(B + \bar{C})(A + \bar{B})$$

- Standard POS: It is an expression where all the variables are present in each sum terms. Each sum terms are called max terms (M_i).

$$(\bar{A} + B + C)(A + \bar{B} + \bar{C})$$

- Conversion of POS to Standard POS
 - Step1: Add to each non-standard product terms a term made up of the product of the missing variable and its complement. This does not change the expression as we are just adding a 0.
 - Step2: Apply rule 12: $A + BC = (A + B)(A + C)$
 - Step3: Repeat step 1 until all the sum terms contain all the variable in the domain.
- Product-of-Sum is used to describe when the function is 0.

Convert the following Boolean expression into standard SOP form:

$$A\bar{B}C + \bar{A}\bar{B} + AB\bar{C}D$$

Convert the expression $W\bar{X}Y + \bar{X}Y\bar{Z} + WX\bar{Y}$ to standard SOP form.

Convert the following Boolean expression into standard POS form:

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

Convert the expression $(A + \bar{B})(B + C)$ to standard POS form.

Min Terms and Max Terms

- Each variable in a Boolean expression is a literal. —
- Boolean variable can appear in normal (A) or complemented (\bar{A}) form.
- Each product of all variables in the domain is called Min-Term.
- Each sum of all variables in the domain is called Max-Term.

A	B	C	Min-Terms	
0	0	0	$\bar{A}\bar{B}\bar{C}$	m_0
0	0	1	$\bar{A}\bar{B}C$	m_1
0	1	0	$\bar{A}B\bar{C}$	m_2
0	1	1	$\bar{A}BC$	m_3
1	0	0	$A\bar{B}\bar{C}$	m_4
1	0	1	$A\bar{B}C$	m_5
1	1	0	$AB\bar{C}$	m_6
1	1	1	ABC	m_7

For Min-Terms:

When 0 \rightarrow Complemented Form

When 1 \rightarrow Normal Form

A	B	C	Max-Terms	
0	0	0	$A + B + C$	M_0
0	0	1	$A + B + \bar{C}$	M_1
0	1	0	$A + \bar{B} + C$	M_2
0	1	1	$A + \bar{B} + \bar{C}$	M_3
1	0	0	$\bar{A} + B + C$	M_4
1	0	1	$\bar{A} + B + \bar{C}$	M_5
1	1	0	$\bar{A} + \bar{B} + C$	M_6
1	1	1	$\bar{A} + \bar{B} + \bar{C}$	M_7

For Max-Terms:

When 1 \rightarrow Complemented Form

When 0 \rightarrow Normal Form

Boolean Expression(SOP) to Truth-Table

- Truth-table can be formed for any Boolean expression.
- Converting a Boolean Expression to SSOP can make this task a lot easier.
- Find the truth-table for the following Boolean expression:

$$F(A, B, C) = AB + \bar{B}\bar{C}$$

$$F(A, B, C) = AB(C + \bar{C}) + (A + \bar{A})\bar{B}\bar{C}$$

$$F(A, B, C) = \underline{ABC + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}}$$

A	B	C	Min-Terms
0	0	0	$\bar{A}\bar{B}\bar{C}$
0	0	1	$\bar{A}\bar{B}C$
0	1	0	$\bar{A}B\bar{C}$
0	1	1	$\bar{A}BC$
1	0	0	$A\bar{B}\bar{C}$
1	0	1	$A\bar{B}C$
1	1	0	$AB\bar{C}$
1	1	1	ABC



A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Truth-Table to Function Implementation

- Find and implement the function from the following truth-table.

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



A	B	C	F
0	0	0	$\bar{A}\bar{B}\bar{C}$
0	0	1	
0	1	0	$\bar{A}B\bar{C}$
0	1	1	
1	0	0	
1	0	1	
1	1	0	$AB\bar{C}$
1	1	1	ABC

$$F(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + AB\bar{C} + ABC$$

$$F(A, B, C) = \bar{A}\bar{C} + AB$$

- For the function $F = \sum(2,3,5,7)$:
 - Construct the truth table.
 - Implement the function.

Boolean Expression(POS) to Truth-Table

- Form a truth-table for the following Boolean expression.

$$F(A, B, C) = (A + B) \cdot (\bar{B} + \bar{C})$$

- In the first step, we will convert the POS to SPOS:

$$F(A, B, C) = (A + B + C\bar{C}) \cdot (\bar{B} + \bar{C} + A\bar{A})$$

$$F(A, B, C) = (A + B + C) \cdot (A + B + \bar{C}) \cdot (\bar{B} + \bar{C} + A) \cdot (\bar{B} + \bar{C} + \bar{A})$$

- Once we have converted the expression to SPOS, now we can directly form the truth-table.

A	B	C	Max-Terms
0	0	0	$A + B + C$
0	0	1	$A + B + \bar{C}$
0	1	0	$A + \bar{B} + C$
0	1	1	$A + \bar{B} + \bar{C}$
1	0	0	$\bar{A} + B + C$
1	0	1	$\bar{A} + B + \bar{C}$
1	1	0	$\bar{A} + \bar{B} + C$
1	1	1	$\bar{A} + \bar{B} + \bar{C}$



A	B	C	Max-Terms
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Function Implementation using POS

- For the function $F = \prod(1,2,5,6)$:
 - Construct the truth table.
 - Implement the function.

Solution:

Step 1

A	B	C	Max-Terms
0	0	0	
0	0	1	0
0	1	0	0
0	1	1	
1	0	0	
1	0	1	0
1	1	0	0
1	1	1	

Step 2

A	B	C	Max-Terms
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Step 3

$$F(A, B, C) = \underline{\bar{A}\bar{B}\bar{C}} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$

- Now that we have the Boolean expression, we can simplify it and implement it.

Connecting the Dots between SOP and POS

- From the truth table determine the standard SOP expression and the equivalent POS expression.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Standard SOP expression:

- Write down the sum of min terms of the combinations for which the function is 1.

$$F = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

Equivalent POS expression:


- Write down the product of max terms of the combinations for which the function is 0.

$$F = (A + B + C) \cdot (A + B + \bar{C}) \cdot (A + \bar{B} + C)$$

HOW DOES THIS EVEN WORK!!!!!!!!!!

Connecting the Dots between SOP and POS

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

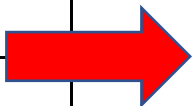

A	B	C	F	\bar{F}
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

$$\bar{F} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C}$$

- Now we have the SOP expression of the complement of the function:

$$\bar{F} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C}$$

- This means we have converted the 0s of the function 1s and vice versa.
- What if we turn the 0s back to 1, that is we convert \bar{F} to F

Connecting the Dots between SOP and POS

$$\bar{F} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C}$$

- Now to convert the 0s back to 1s we complement \bar{F} that is $\bar{\bar{F}}$.

$$\bar{\bar{F}} = \overline{\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C}}$$

$$F = \overline{\bar{A}\bar{B}\bar{C}} \cdot \overline{\bar{A}\bar{B}C} \cdot \overline{\bar{A}B\bar{C}}$$

$$F = (A + B + C) \cdot (A + B + \bar{C}) \cdot (A + \bar{B} + C)$$

- So we have reached the same expression of POS as we did earlier.
- SOP is the positive logic definition of the function.
- POS is the negative logic definition of the function.

What is positive logic and what is negative logic????

1. Thomas L. Floyd, “Digital Fundamentals” 11th edition, Prentice Hall – Pearson Education.

Thank You