



American International University-Bangladesh (AIUB)
Faculty of Engineering

DIGITAL LOGIC AND CIRCUITS

OBE Assignment [30 marks]

Summer Semester 2020-21

Submission Deadline: 08.08.2021

Submission Link: <https://forms.gle/8H8gDqCtH7YXvX8j7>

| | | |
|-----|---|----------|
| CO3 | Formulate solutions of a complex engineering problem with conflicting requirements by applying information, concepts and procedures in engineering fundamentals of digital logic and circuits at gate and transistor level. | P.a.3.C3 |
|-----|---|----------|

Recently you have been registered for COVID-19 vaccination. In the vaccination center, only 4 people are allowed in a queue with maintaining three feet distance in front of a small room. If more than 2 people enter the room at the same time an alarm goes off. Each awaiting applicant has one digital token with sensor to detect their presence in the room.

Your task is to:

- Outline the necessary steps in correct sequence of the standard procedure to design a digital system and design the system. Also show the outlined steps, which will trigger the alarm and implement the system with CMOS logic.
- The human audible ranges from 20Hz – 20kHz. However, any sound below 250Hz is considered to be disturbingly low pitched and any sound above 4500Hz is considered to be disturbingly high pitched. Design the alarm timer circuit with a frequency of **M5 Hz** and a duty cycle of **N%** [where **M = C+O+V+I+D** and **N = 100 – M**]. However, if M5 Hz is not within soothing hearing limits, take frequency, $f = 400\text{Hz}$. Choose the capacitor value from the given list based on the suitability of your requirements. ($C = 50\mu\text{F}/250\mu\text{F}/470\mu\text{F}$)

Direction: The numbers **COVID** are the middle five digits of your ID (SS-**COVID**-S)
(In case the last two letters of your ID is 00, use 36 instead.)

Submission Guidelines:

- ** The assignment should only be **submitted in the proper link**.
- ** The assignment will **not be accepted after the submission deadline**.
- ** You **MUST** write your **CLASS SERIAL, ID, NAME, PAGE NUMBER** on top of the page.
- ** The assignment **MUST** be submitted in **PDF** format.
- ** Any trace of **copying will result in 0** for that section.



American International University-Bangladesh (AIUB)
Faculty of Engineering

MARKING RUBRIC:

| CP | Assessment Criteria | Evaluation Criteria | | | | Marks |
|----------------------|--|---|---|--|---|-------|
| | | Poor [1-4] | Average [5-6] | Good [7-8] | Excellent [9-10] | |
| K3, P1 | Outline of the standard procedure of digital system design | More than three steps are incorrect or missing and not in correct sequence | One or Two steps of the standard procedure is missing with a one or two steps not in sequence. | All the steps of the procedure have been identified with one or two steps not in correct sequence | All the steps of the procedure have been identified and in correct sequence | |
| | Digital Triggering Circuit Design. | Design flow has major errors and transistor level design has major flaws. | Design Flow has major error with error carried forward to transistor level design | Design Flow has minor error with error carried forward to transistor level design | Accurate Design Flow with transistor level design having no or minor errors | |
| P2, P6 | Alarm/ Buzzer Design | Alarm design has major flaws which does not comply with the conflicting requirements with major calculation errors. | Alarm design has major flaws which does not comply with the conflicting requirements but with minor calculation errors. | Alarm design is correct and complies to the conflicting requirements but, with major calculation errors. | The alarm design is correct and comply to the requirements with no or minor calculation errors. | |
| Total Marks Obtained | | | | | | |