



American International University- Bangladesh  
Department of Electrical and Electronic Engineering  
EEE 3102: Digital Logic & Circuits Laboratory

**Title:** Design of adder, subtractor and comparator circuits.

**Abstract:**


The purpose of this experiment is to learn the design and behaviour of adder, subtractor and comparator logic circuits. Adders and subtractors are the most basic and most important part of digital electronics.

**Part I (Adder and Subtractor):**

Adders and subtractors are digital circuits which are capable of adding and subtracting binary digits. They are the most important part in the design of Arithmetic Logic Unit (ALU). In this experiment different types of adders and subtractors will be designed and their behavior will be observed.

**Theory and Methodology:**

An adder or summer is a combinational circuit that adds binary numbers. There are mainly two kinds of adders, half adder and full adder. The half adder can add only two single bits of binary digit and outputs the sum of the bits and a carry which is the overflow of the sum. A full adder can add two single bit digits and one carry bit which is the overflow of the sum of the previous stage of addition and outputs the sum and the carry.

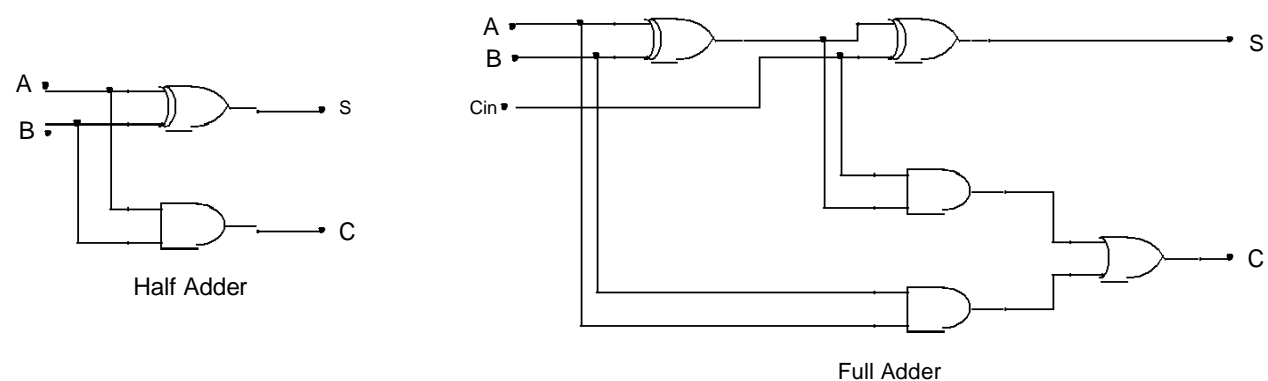

**Fig.1.1:** Schematics of Half Adder and Full Adder

The Boolean expression for half and full adder is given below –

Half adder–

$$S = A \oplus B$$

$$C_{out} = AB$$

Full adder –

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = C_{in} (A \oplus B) + AB$$



The Boolean expressions for half and full subtractor are given below –

Half subtractor –

$$D = X \oplus Y$$

$$B = X'Y$$

Full subtractor –

$$D = X \oplus Y \oplus \text{Bin}$$

$$\text{Bout} = X'Y + X'\text{Bin} + Y\text{Bin}$$

Truth table for half subtractor –


X	Y	D	B
0	0		
0	1		
1	0		
1	1		

Truth table for full subtractor –

X	Y	Bin	D	B
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

### Using Full Adder blocks for addition of n- bit systems:

Full adder blocks can be connected for summation of n-bit systems. To design a 2 bit full adder, two 1 bit full adders are connected in parallel connection as shown in the figure below. The same process can be used for designing n-bit Full Adder for addition of words having a length of n-bits.

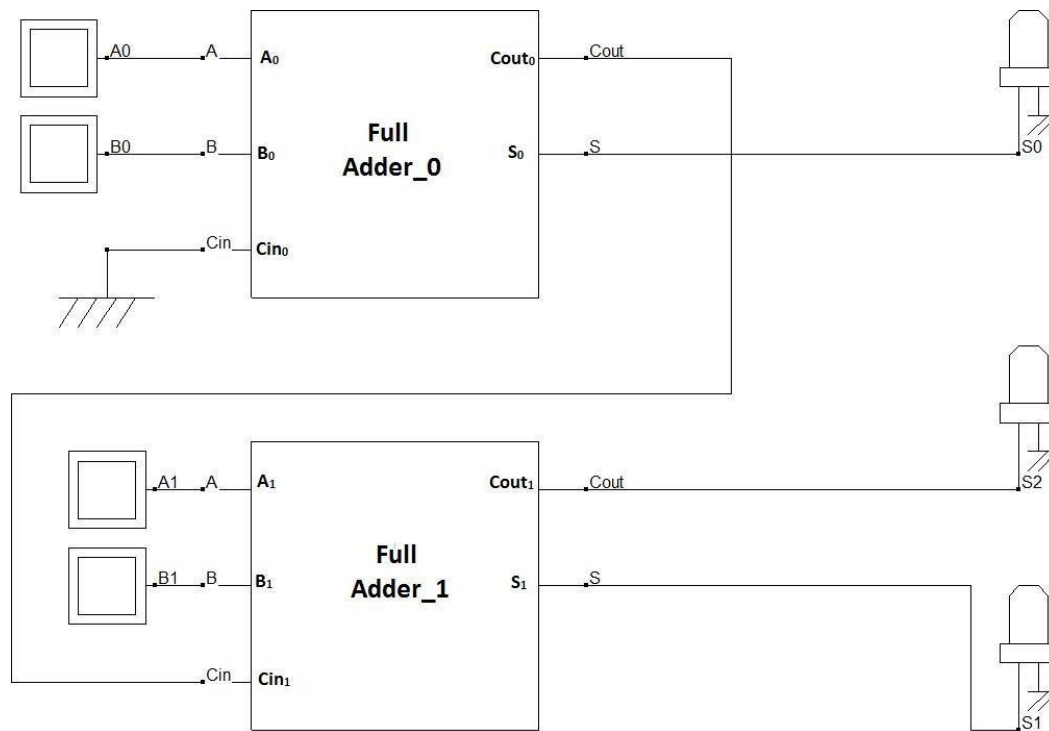


**Fig. 1.3:** 2-bit Full adder design using 1 bit full adder blocks

Here, the LSB of both word A and B ( $A_0$  and  $B_0$ ) are connected in the first stage full adder block and  $Cin$  of this block ( $Cin_0$ ) is connected to ground (as there is no carry in available at the initial stage). The MSB of both word A and B ( $A_1$  and  $B_1$ ) are connected in the first stage full adder block and  $Cin$  of this block ( $Cin_1$ ) is connected to the previous stage  $Cout$  ( $Cout_0$ ). Summation output for the LSB is available from the first stage Sum ( $S_0$ ). The next stage block outputs Sum ( $S_1$ ) and Carry out ( $Cout_1$ ) provide the MSBs for the next stage output ( $S_1$  and  $S_2$ ).

**Part II (Comparator):** A magnitude comparator is a device that takes in two sets of inputs in its input and compares them to provide an output, if they are equal, greater than or less than the other. In this experiment 1-bit comparator will be designed at first and using the 1-bit comparator block, 2-bit comparator will be designed.

**Theory and Methodology:** Magnitude Comparators are combinational logic circuits that take 2 sets of data as its inputs and tests whether the value represented by one binary word is greater than, less than, or equal to the value represented by another binary word.

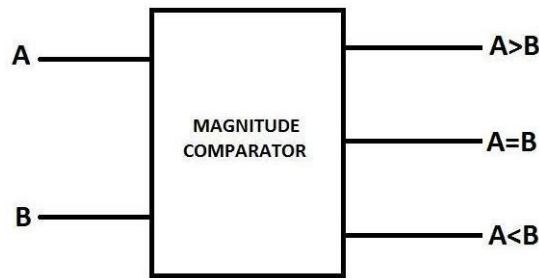

**Fig.2.1:** Block Diagram of 1 Bit Magnitude Comparator

Depending on the input combination for a 1-bit magnitude comparator, following behavior table can be developed using the logic expressions.

**A=B** if, A=B=0 or A=B=1;  
**A>B** if A=1 and B=0;  
**A<B** if A=0 and B=1;

		A=B	A>B	A<B
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

The SOP expressions for the output lines can be written as

$$\begin{aligned}(A=B) &= A'B' + AB; \\ (A<B) &= AB'; \\ (A>B) &= A'B;\end{aligned}$$

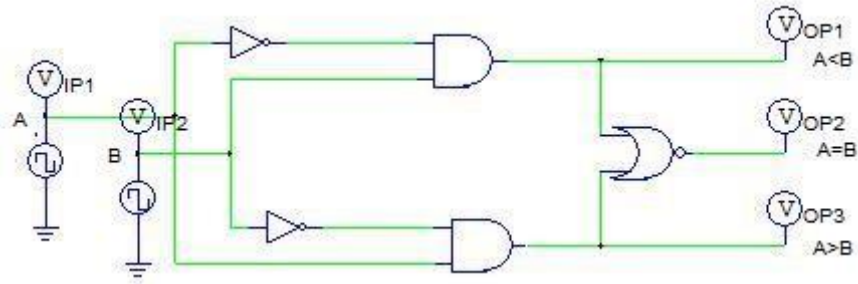


Fig.2.2: 1-Bit Comparator

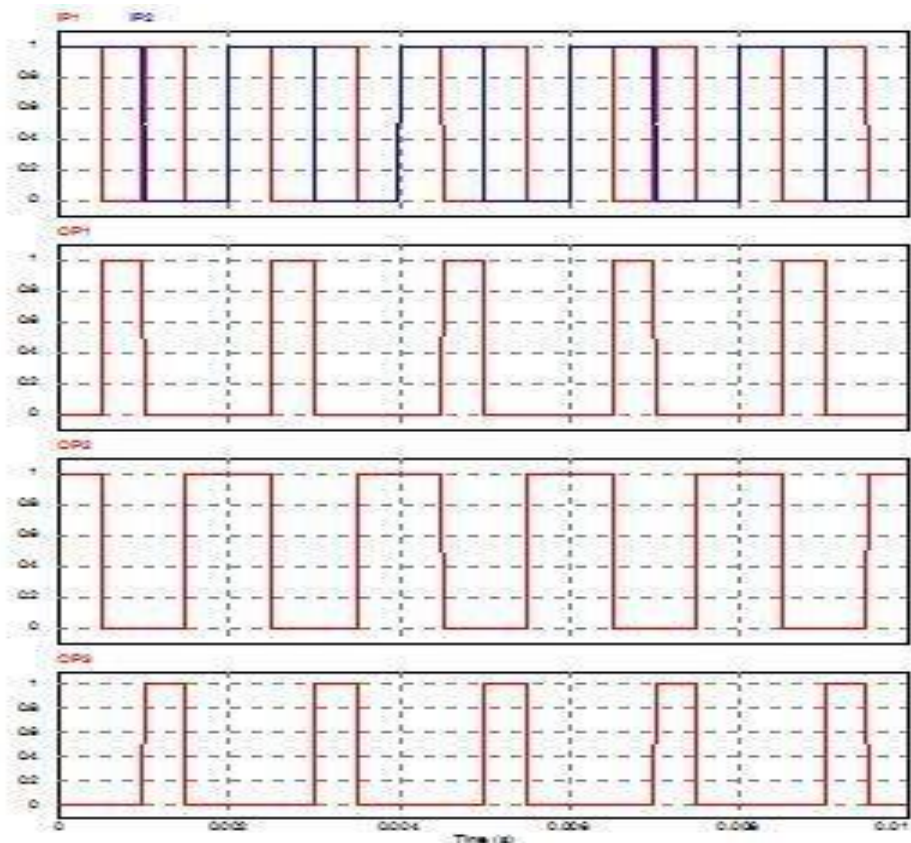


Fig.2.3: Timing Diagram for 1-Bit

**Comparator 2 Bit Comparator design using 1 bit block:**

Using 1-bit blocks, n-bit Magnitude comparator can be designed.

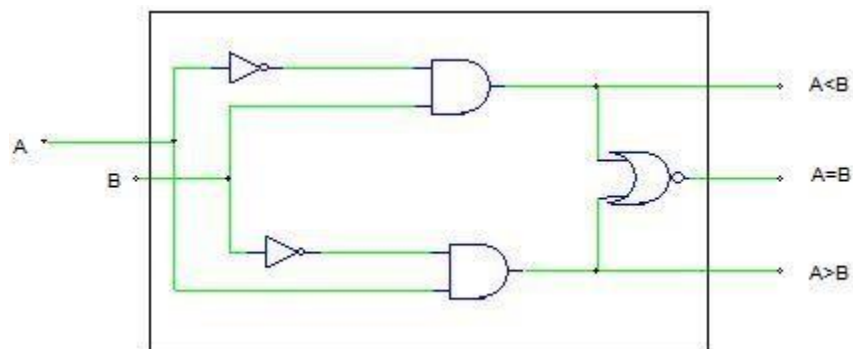


Fig.2.4: 1-Bit Comparator Block

**Designing a 2-bit comparator using 1-bit blocks:**

Let us consider 2 words,

**Word A** ->  $A_1A_0$

**Word B** ->  $B_1B_0$

For comparing, the following process is used as writing the logic equations.

**For  $A=B$ ,**

If  $(A_1=B_1) \& (A_0=B_0)$ , then  $(A=B)$ ;

**For  $A>B$ ,**


If  $(A_1>B_1)$  then  $(A>B)$  or

if  $(A_1=B_1) \& (A_0>B_0)$ , then  $(A>B)$ ;

**For  $A<B$ ,**

If  $(A_1<B_1)$  then  $(A<B)$  or

if  $(A_1=B_1) \& (A_0<B_0)$ , then  $(A<B)$

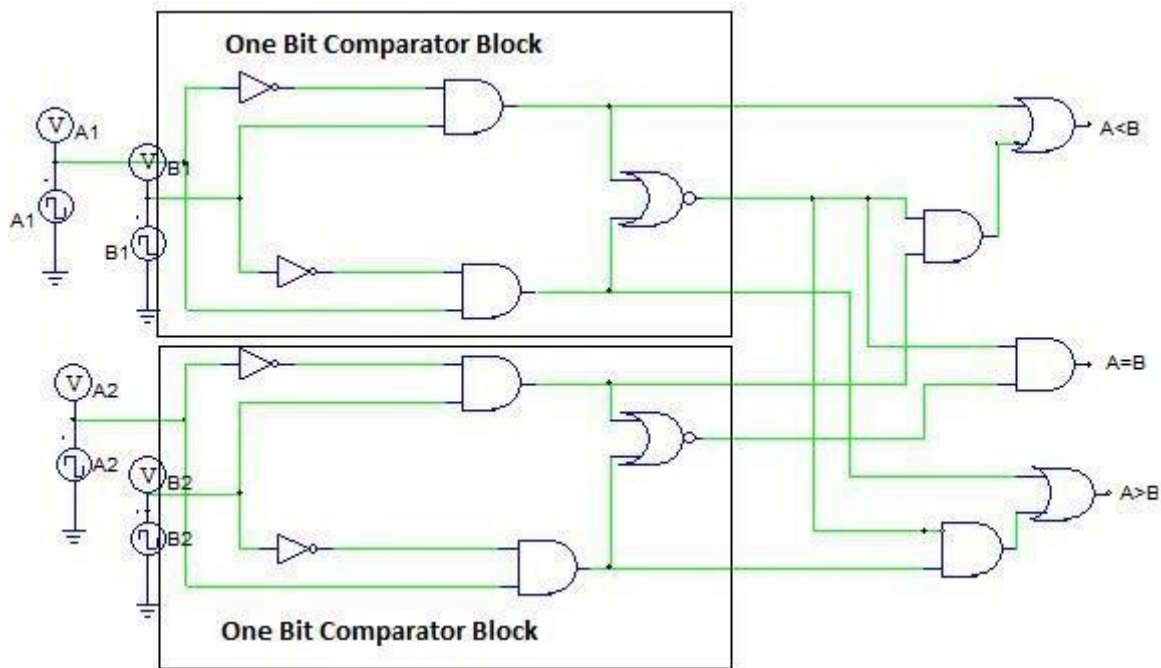

**Fig.2.5:** 2-Bit Comparator using 1\_bit Comparator Block

For designing a 2-bit comparator using 1-bit comparator block, 2 1-bit comparator block, 3 AND gate and 2 OR gate is needed as shown in Fig.4.

**Pre-Lab Homework:**

Read about the characteristics of adder and subtractor circuits from any book or websites and use PSIM to generate the output of the circuits provided in this lab sheet. Save the simulation results and bring it to the lab.

**Apparatus:**

1. Digital trainer board
2. IC 7408:2 pcs
3. IC 7404:2 pcs
4. IC 7486:2 pcs
5. IC 7431:2 pcs
6. IC 7483:1 pcs
7. Connecting wires

**Precautions:**

1. Make sure that all the LEDs and the toggle switches of the trainer board are working properly.
2. Do not short any connections. Short connection can produce heat (due to high current flow) which is harmful for the components.

**Experimental Procedure:**

1. Determine the output and the truth tables of the logic circuits for full adder and half subtractor given in the theory and methodology part.
2. Determine which gates and how many of them are required, check and detect all the IC numbers.
3. Carefully place the ICs on the Trainer Board and bias them by connecting them to the +5 volt DC supply and ground.
4. Connect those using wires according to the logic diagram; connect the outputs to the LEDs.
5. Check and note down the outputs by giving different inputs according to the derived truth table.
6. Design a 4 bit full adder using IC 7483 and verify its operation.

**Simulation and Measurement:** Compare the experimental data with the simulation results and comment on the differences (if any).

**Report:**

1. Design a full adder circuit for performing 3 bit binary addition.
2. Design a full subtractor circuit for performing 3 bit binary subtractor.
3. Design an 8 bit full adder using 4 bit full adder IC 4008 from PSIM.
4. Design a comparator circuit for comparing two words, each of 3 bits of input using 1 bit block.

**Discussion and Conclusion:**

Interpret the data/findings and determine the extent to which the experiment was successful in complying with the goal that was initially set. Discuss any mistake you might have made while conducting the investigation and describe ways the study could have been improved.


**Reference:**

<http://www.circuitstoday.com/half-adder-and-full-adder>



## **Appendix:**

Pin configuration of IC 74LS83

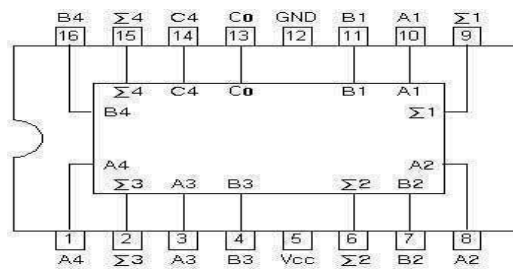

**Fig. : 4-bit Full Adder IC pin configuration**

**Pin configuration for IC-74LS85**

