




# Digital Logic Design


## Multiplexer & De-Multiplexer
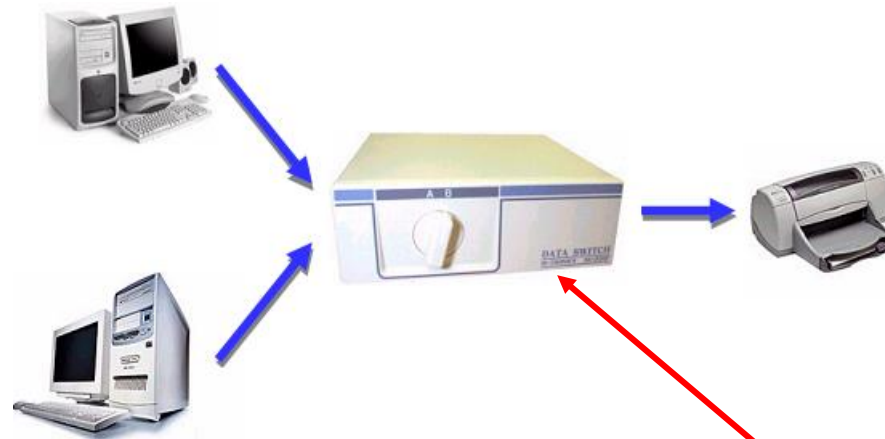
# Multiplexer or Mux or Data Selector

- In the old days, several machines could share an I/O device with a **Switch**.
- The **Switch** allows one computer's output to go to the printer's input.




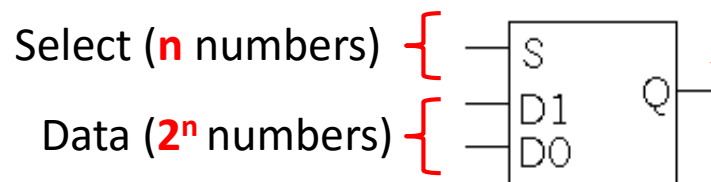- Here is the circuit similar to that printer switch. Multiplexer (Mux)



- This is a 2-to-1 multiplexer or mux.
- The multiplexer routes one of its data inputs (D0 or D1) to the output Q, based on the value of S:

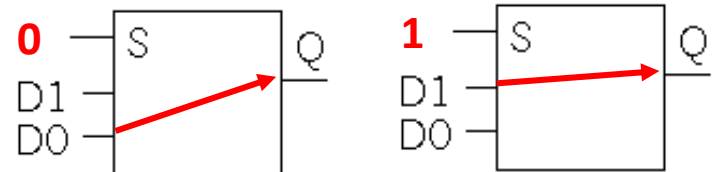- If **S=0**, then D0 is the output (**Q=D0**).
- If **S=1**, then D1 is the output (**Q=D1**).



# Truth table abbreviations, Block diagram and Circuit

- Truth table:

S	D1	D0	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



S	Q
0	D0
1	D1

$$Q = S' D0 + S D1$$

When **S=0**

$$Q = 0' D0 + 0 D1$$

$$Q = 1 D0 + 0$$

$$Q = D0$$




When **S=1**

$$Q = 1' D0 + 1 D1$$


$$Q = 0 D0 + 1 D1$$

$$Q = D1$$

- Block Diagram:

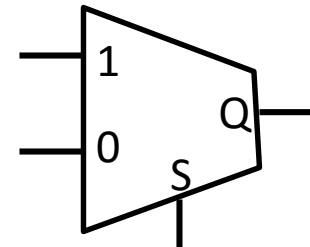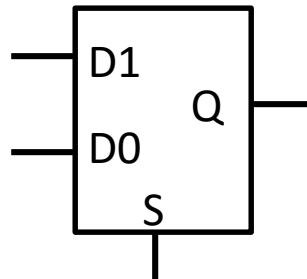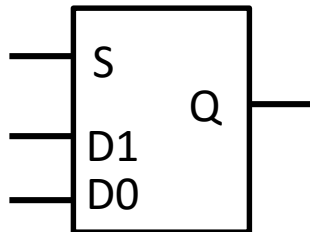


- Circuit Diagram:

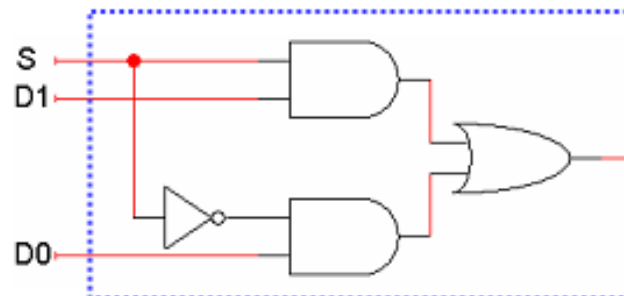

$$Q = S' D0 + S D1$$
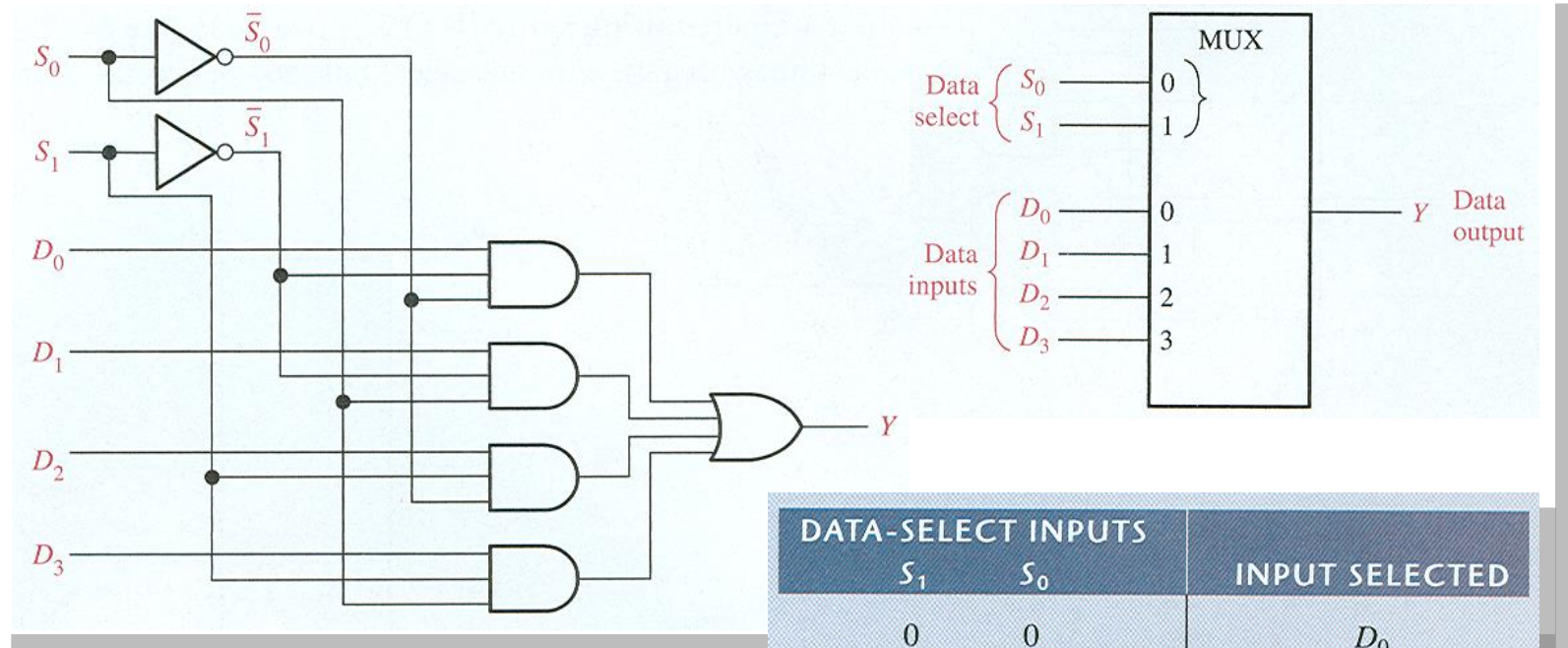
## 4-input multiplexer


- Here is a block diagram and abbreviated truth table for a 4-to-1 mux, which directs one of four different inputs to the single output line.
  - There are four data inputs, so we need *two* bits,  $S_1$  and  $S_0$ , for the mux selection input.



$$Q = S_1'S_0'D_0 + S_1'S_0 D_1 + S_1 S_0'D_2 + S_1 S_0 D_3$$


DATA-SELECT INPUTS		INPUT SELECTED
$S_1$	$S_0$	
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

## Timing Diagram

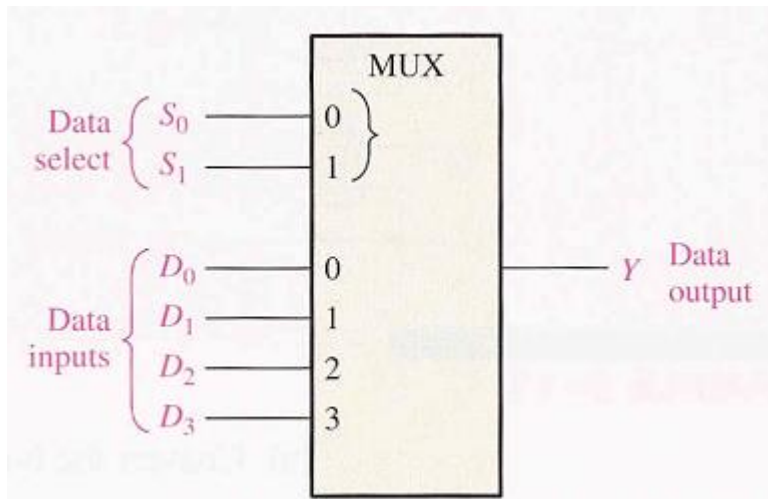


$$Y = D_0 \bar{S}_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 \bar{S}_0 + D_3 S_1 S_0$$

DATA-SELECT INPUTS		INPUT SELECTED
$S_1$	$S_0$	
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

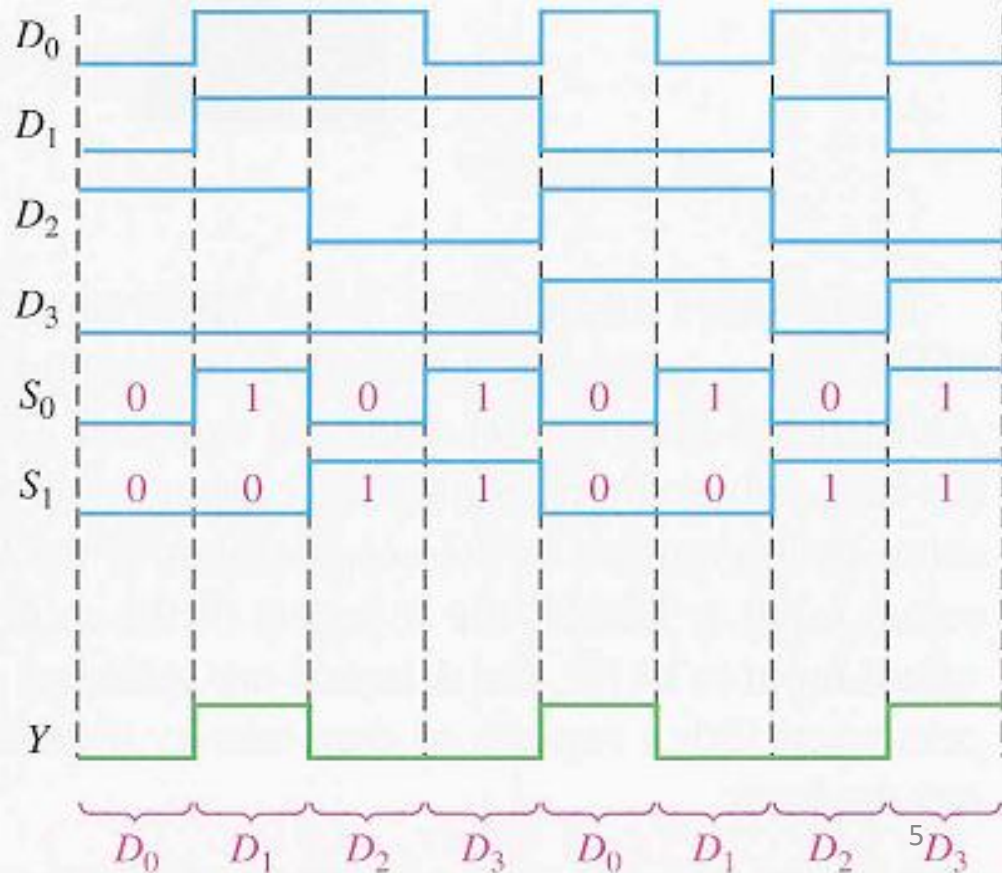
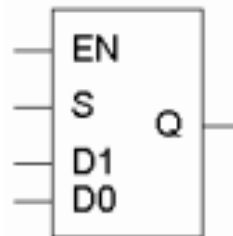
## Enable inputs

- Many devices have an additional **enable input**, which “activates” or “deactivates” the device.
- We could design a 2-to-1 multiplexer with an enable input that’s used as follows.
  - EN=0 disables the multiplexer, which forces the output to be 0. (It does *not* turn off the multiplexer.)
  - EN=1 enables the multiplexer, and it works as specified earlier.
- Enable inputs are especially useful in combining smaller muxes together to make larger ones, as we’ll see later today.



EN	S	D1	D0	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1



## Truth table abbreviations

EN	S	D1	D0	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

- Notice that when EN=0, then Q is always 0, regardless of what S, D1 and D0 are set to.
- We can shorten the truth table by including Xs in the input variable columns, as shown on the bottom right.



EN	S	D1	D0	Q
0	x	x	x	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

## Another abbr. 4 U

- Also, when  $EN=1$  notice that if  $S=0$  then  $Q=D0$ , but if  $S=1$  then  $Q=D1$ .
- Another way to abbreviate a truth table is to list input variables in the output columns, as shown on the right.

EN	S	D1	D0	Q
0	x	x	x	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1




EN	S	Q
0	x	0
1	0	D0
1	1	D1

- This final version of the 2-to-1 multiplexer truth table is much clearer, and matches the equation  $Q = S'D0 + S D1$  very closely.




## 8-to- 1 Mux using ONLY 4-to-1 Mux

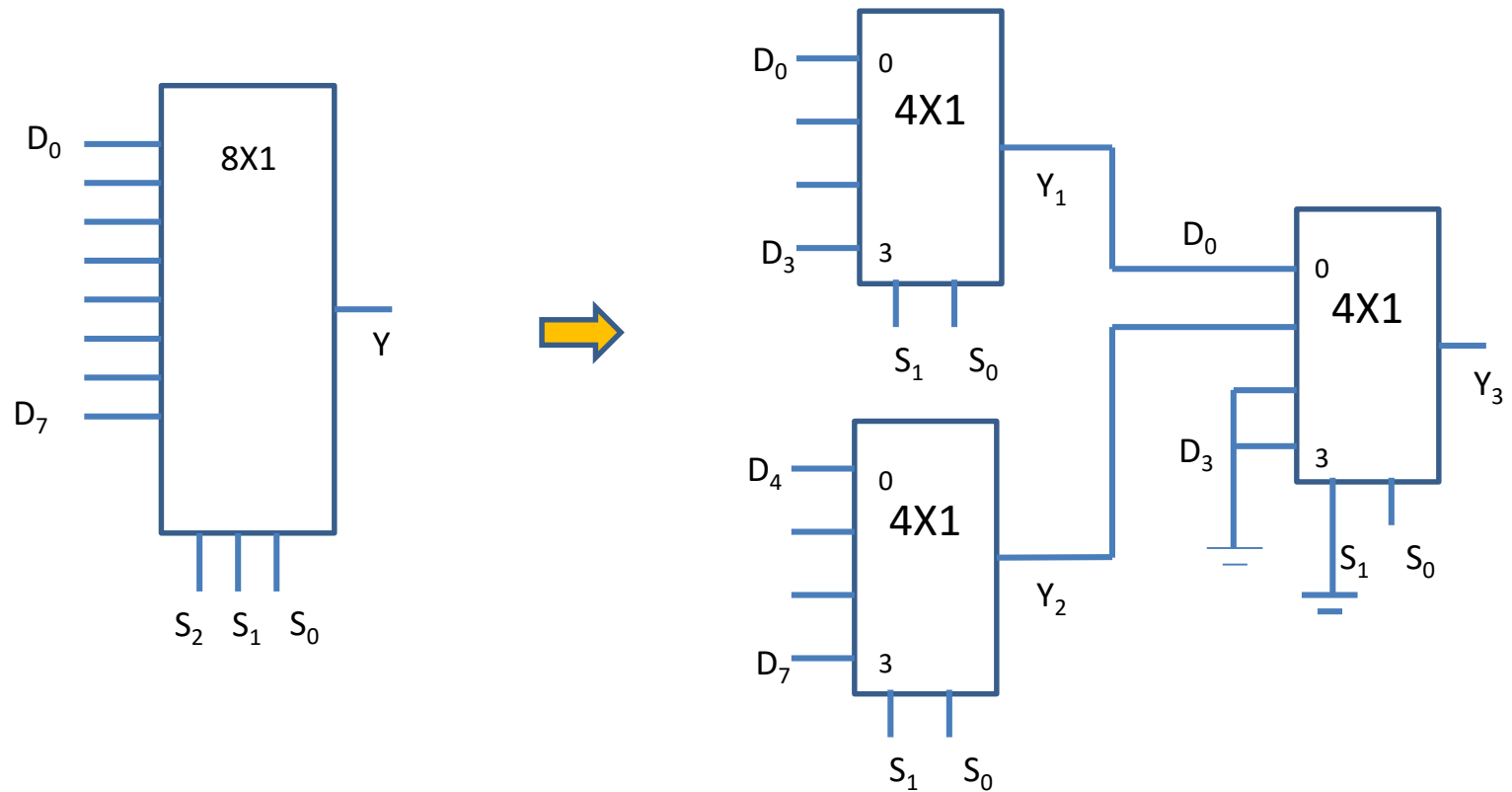

## Implementing functions with multiplexers

- Muxes can be used to implement arbitrary functions.
- One way to implement a function of  $n$  variables is to use an  $2^n$ -to-1 mux:
- For example, let's look at  $f(x,y,z) = \Sigma(1,2,6,7)$ .

x	y	z	f
0	0	0	0 → D0
0	0	1	1 → D1
0	1	0	1 → D2
0	1	1	0 → D3
1	0	0	0 → D4
1	0	1	0 → D5
1	1	0	1 → D6
1	1	1	1 → D7

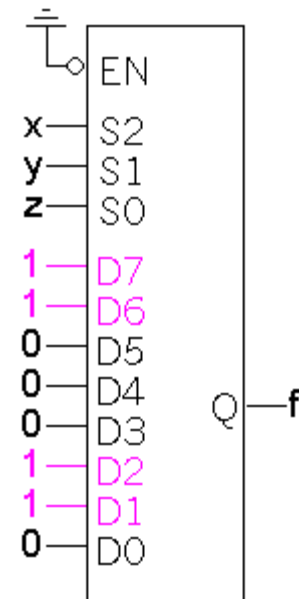



# MULTIPLEXER

## Boolean Function Implementation ([advanced](#))

**Question:** Implement the following function with **only one 4-to-1** multiplexer:

$$F(A,B,C) = \Sigma (1, 3, 5, 6)$$

For **3 variables**, it takes:

- a) **One** 8-to-1 Mux, or
- b) **Three** 4-to-1 Mux


**Only ONE 4-to-1 ..???**

## Procedure:

- 1) Implement the truth table,
- 2) Write the SOP expression in the decimal format,  $F(A,B,C) = \Sigma (1, 3, 5, 6)$
- 3) If the Boolean function has  $n+1$  Variables, then connect  $n$  of these variables to the select lines of a MUX maintain the order.
- 4) Based on the select lines, find the total number of input lines for the MUX. The remaining variable will be used for the inputs of the MUX.

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$F(A,B,C) = \Sigma (1, 3, 5, 6)$$

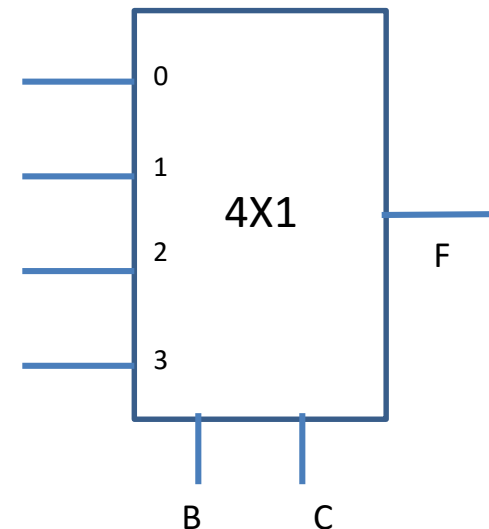

- Consider now the single variable **A**. It can either be **0** or **1**.
- From the truth table, find the minterms for which **A** is **0**. The minterms are 0, 1, 2 & 3.
- From the truth table, find the minterms for which **A** is **1**. The minterms are 4, 5, 6 & 7.

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>
A'	0	1	2	3
A	4	5	6	7

- List the inputs of the MUX and under them list all the minterms in two rows.
- The first row lists all those minterms where **A** is **0**, and the second row all the minterms with **A** is **1**.

- **Circle** all the minterms of the function and inspect **each column** separately.

$$F(A,B,C) = \Sigma (1, 3, 5, 6)$$

	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	1	2	3
$A$	4	5	6	7
	0	1	A	$A'$


- If the two minterms in a column are not circled, **apply 0** to the corresponding MUX input.
- If the two minterms are circled, **apply 1** to the corresponding MUX input.
- If the bottom minterm is circled and the top is not circled, **apply A** to the corresponding MUX input.
- If the top minterm is circled and the bottom is not circled, **apply  $A'$**  to the corresponding MUX input.



$$F(A,B,C) = \Sigma (1, 3, 5, 6)$$

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	1	2	3
A	4	5	6	7
	0	1	A	$A'$

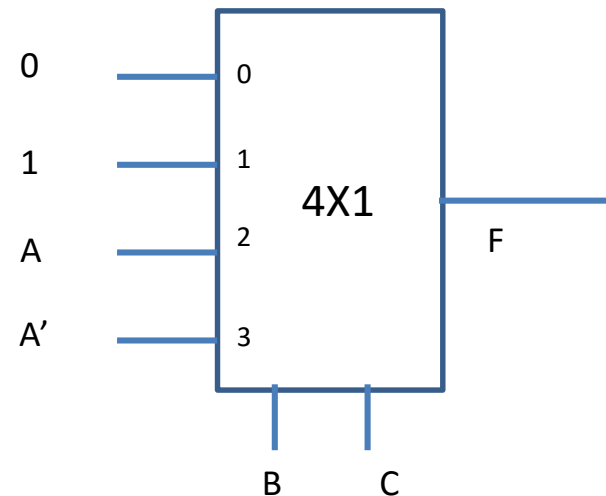


## Example:

Implement the following function with **only one 8-to-1** multiplexer:

$$F(A,B,C,D) = \Sigma (0, 1, 3, 4, 8, 9, 15)$$

	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	0	1	2	3	4	5	6	7
$A$	8	9	10	11	12	13	14	15
	1	1	0	$A'$	$A'$	0	0	$A$

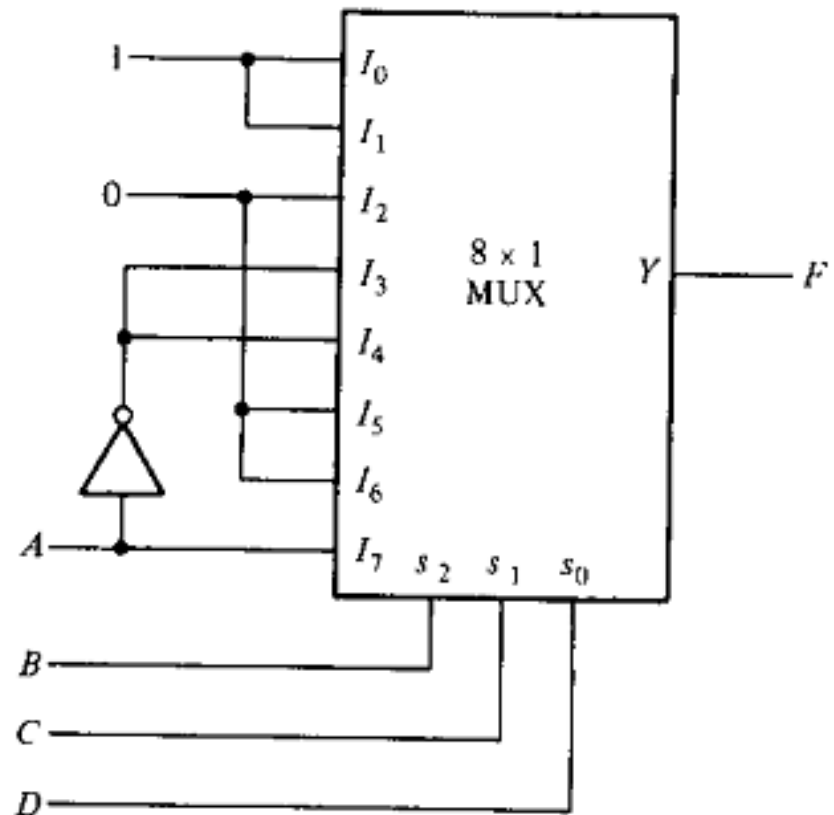


## Example:

Implement the following function using 4x1 MUX:  $F(A,B,C) = \Sigma (2, 3, 4, 6)$

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	0

	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	1	2	3
A	4	5	6	7
	A	0	1	$A'$

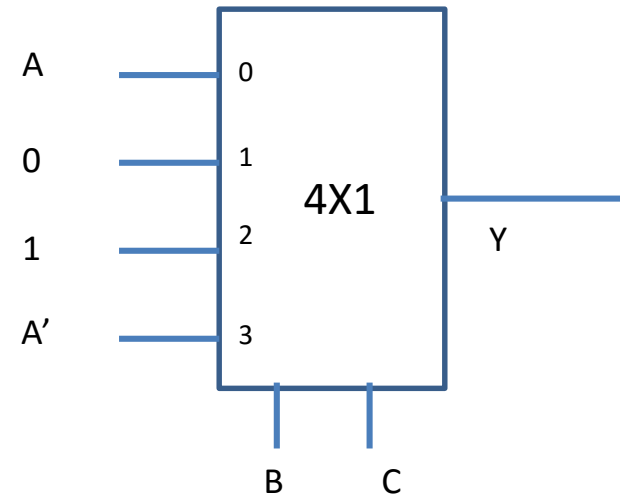


**Example:**


$$F(A,B,C) = \Sigma (2, 3, 4, 6)$$

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	0

	$I_0$	$I_1$	$I_2$	$I_3$
$B'$	0	1	4	5
B	2	3	6	7
	B	B	1	0

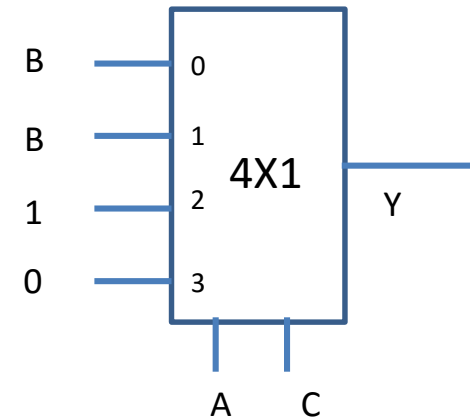

	$I_0$	$I_1$	$I_2$	$I_3$
$C'$	0	2	4	6
C	1	3	5	7
	0	1	$C'$	$C'$

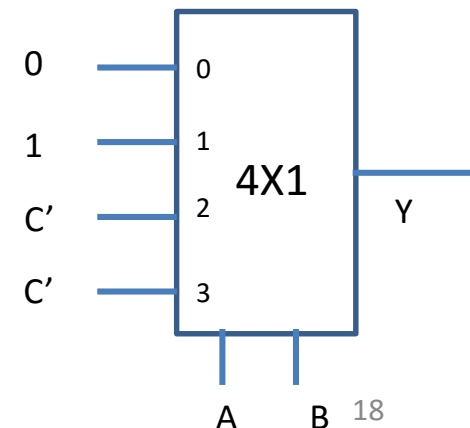

Example:

$$F(A,B,C,D) = \Sigma (0,2,3,6,7,9,12,13,15)$$



	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	0	1	2	3	4	5	6	7
$A$	8	9	10	11	12	13	14	15
	$A'$	$A$	$A'$	$A'$	$A$	$A$	$A'$	1

Example: AND gate

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F(A,B) = AB$$

	$I_0$	$I_1$
$A'$	0	1
$A$	2	3
	0	$A$

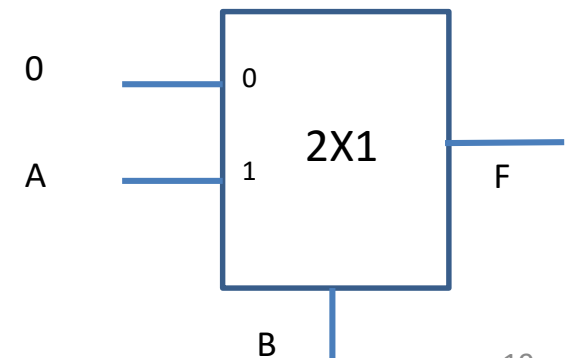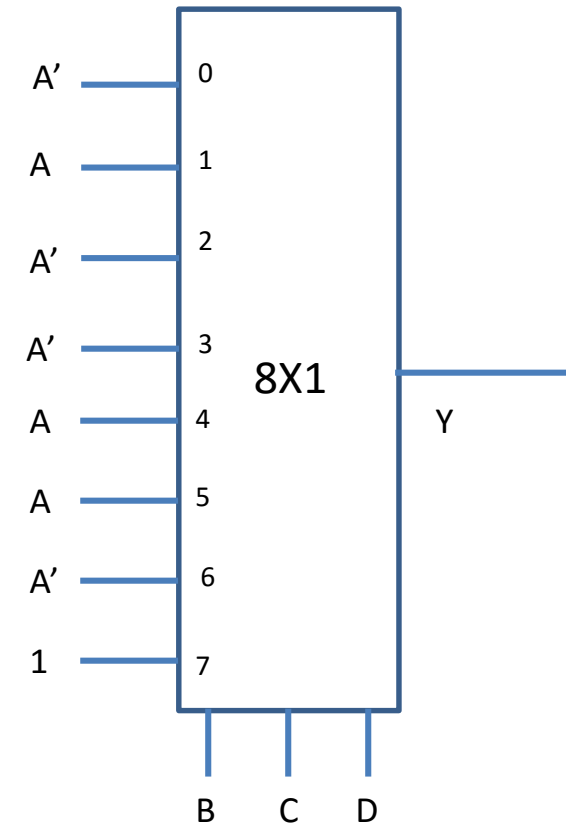

**Example:**

$$F(A,B,C) = AB+BC$$

$$F = AB+BC$$

$$= AB(C+C')+(A+A')BC$$


$$= ABC+ABC'+ABC+A'BC$$

$$= ABC+ABC' +A'BC$$

7      6      3

	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	1	2	3
$A$	4	5	6	7
	0	0	A	1

Minterm	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

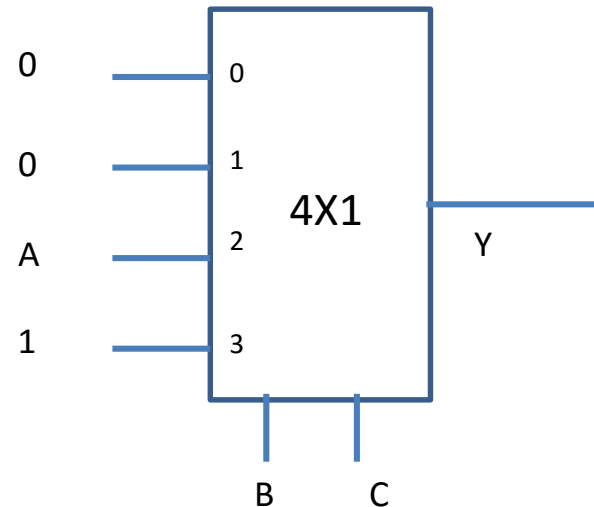



## Summary


- A  $2^n$ -to-1 multiplexer routes one of  $2^n$  input lines to a single output line.
- Just like decoders,
  - Muxes are common enough to be supplied as stand-alone devices for use in modular designs.
  - Muxes can implement arbitrary functions.
- We saw some variations of the standard multiplexer:
  - Smaller muxes can be combined to produce larger ones.
  - We can add active-low or active-high enable inputs.
- As always, we use truth tables and Boolean algebra to analyze things.

# Demultiplexers

## 2-line-to 4-line demux

A **demultiplexer (DEMUX)** basically reverses the multiplexing function. It takes digital information from one line and distributes it to a given number of output lines. For this reason, the demultiplexer is also known as a data distributor. As you will learn, decoders can also be used as demultiplexers.

DATA-SELECT INPUTS		OUTPUT SELECTED
$S_1$	$S_0$	
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

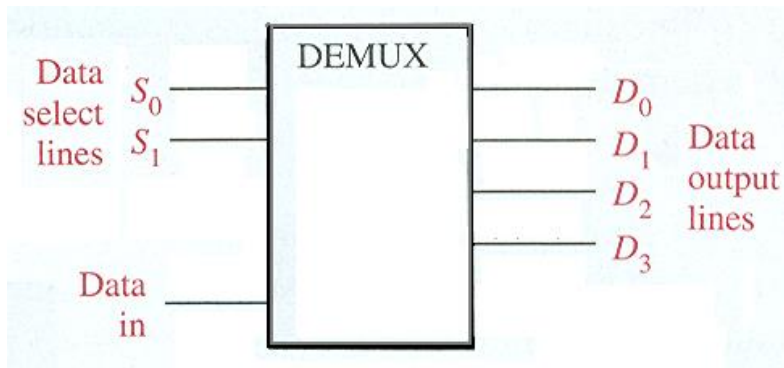


$$D_0 = S_1' S_0' D_{in}$$


$$D_1 = S_1' S_0 D_{in}$$

$$D_2 = S_1 S_0' D_{in}$$


$$D_3 = S_1 S_0 D_{in}$$

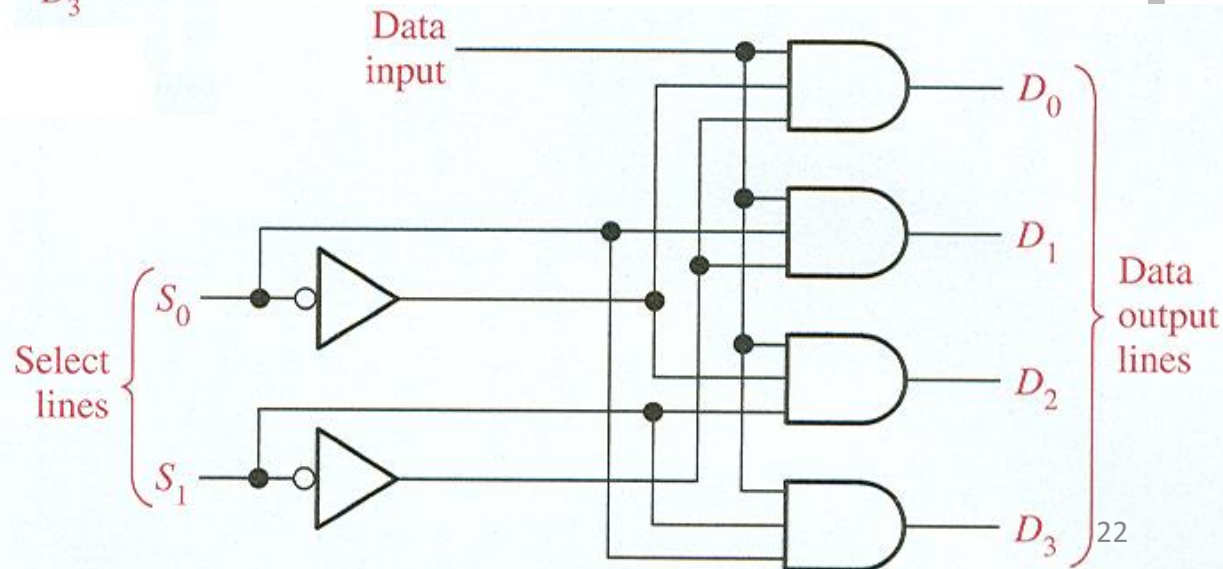

## Timing Diagram


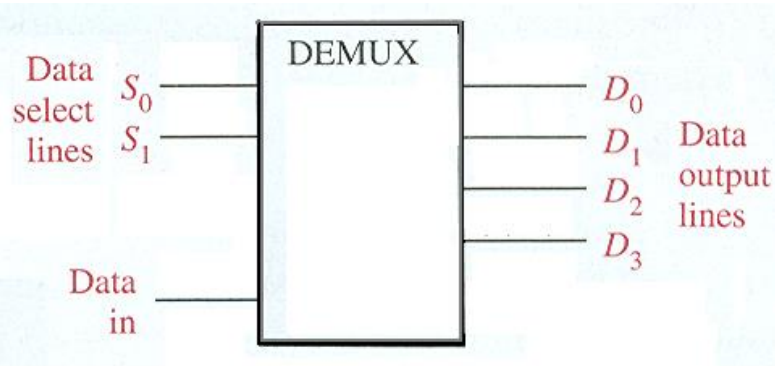


DATA-SELECT INPUTS		OUTPUT SELECTED
$S_1$	$S_0$	
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

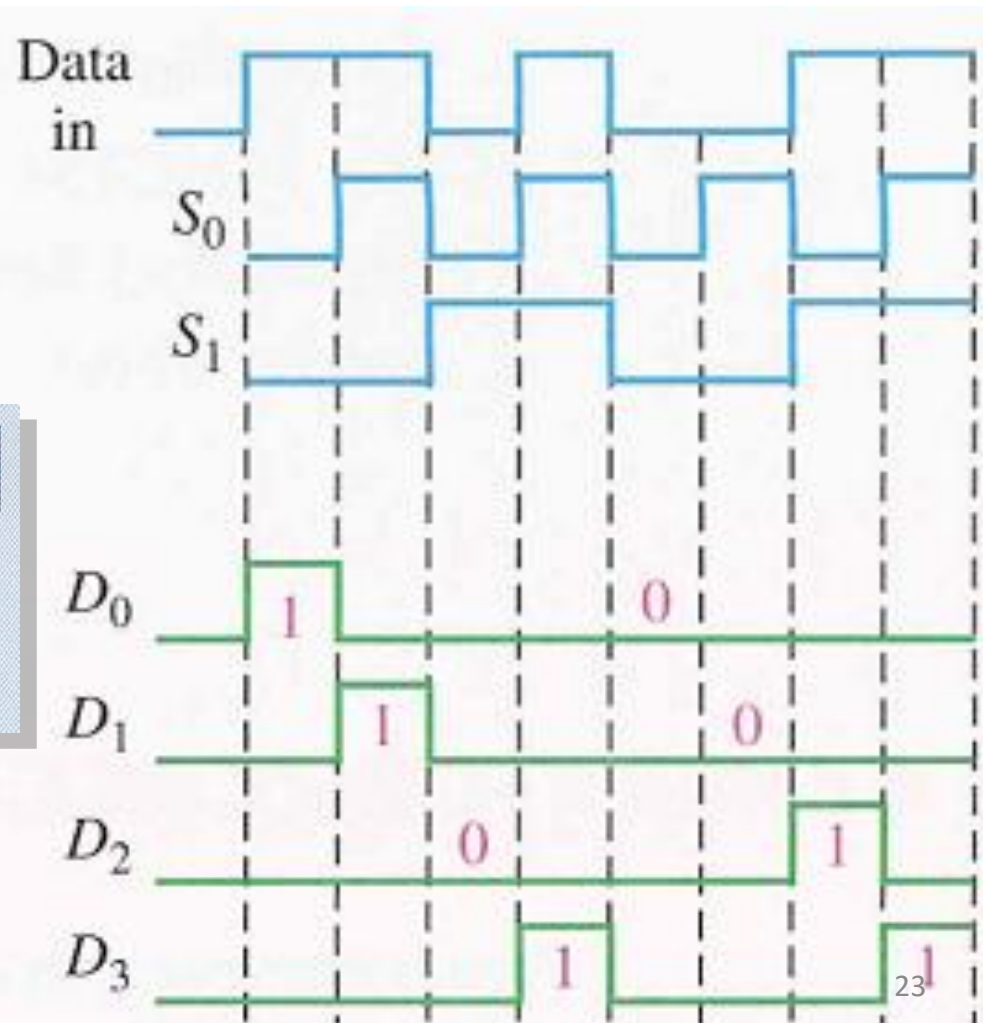

# Cascading DEMUX

Designing a 1x11 DEMUX using 1x2 DEMUX

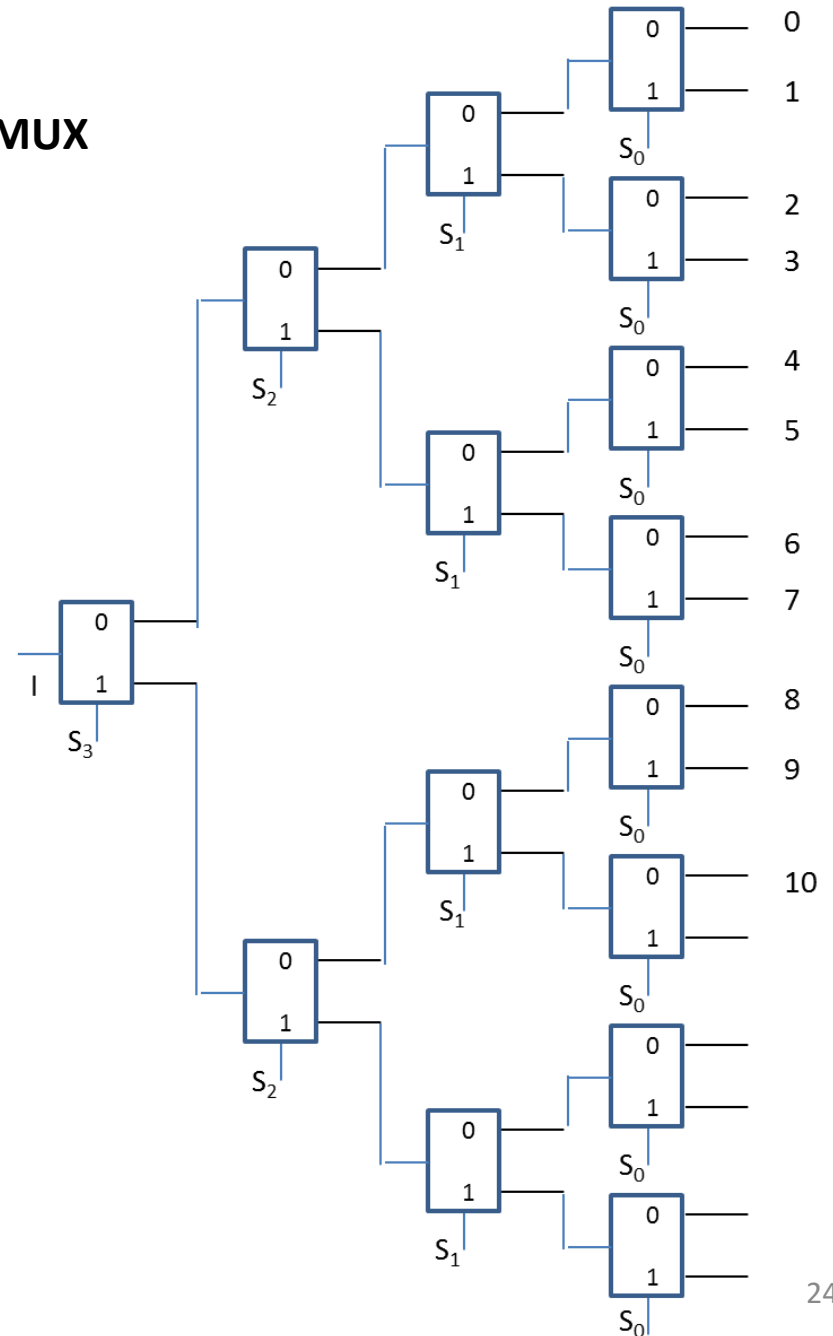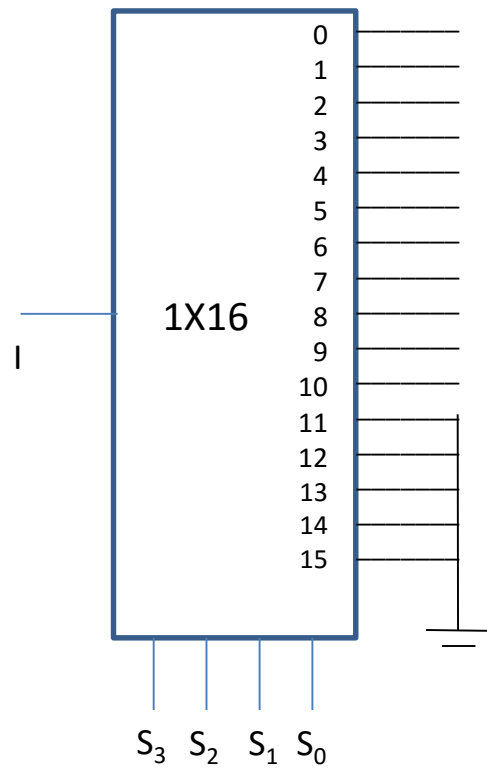



## **Reference:**

**Mixed contents from books by Floyd; Mano; Vahid  
And Howard.**

## **Acknowledgement:**

**Nafiz Ahmed Chisty**

# Thanks