

Lecture -5


Combination Circuits-1

Prepared By: Asif Mahfuz




Adder

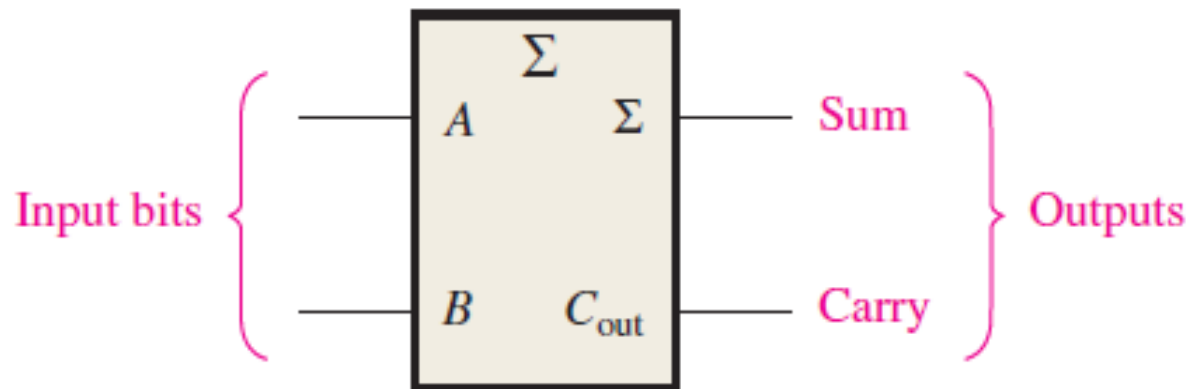- Adders are important in computers and in other digital systems.
- To design an adder we first need to understand the basic adder operation.
- Thus we first need to know the rules of binary addition.
- The rules of binary addition are as follows:
 - $0 + 0 = 0$
 - $0 + 1 = 1$
 - $1 + 0 = 1$
 - $1 + 1 = 10$
- There are two types of adders namely, **Half-adder** and a **Full-adder**.



Block diagram of a Half-Adder

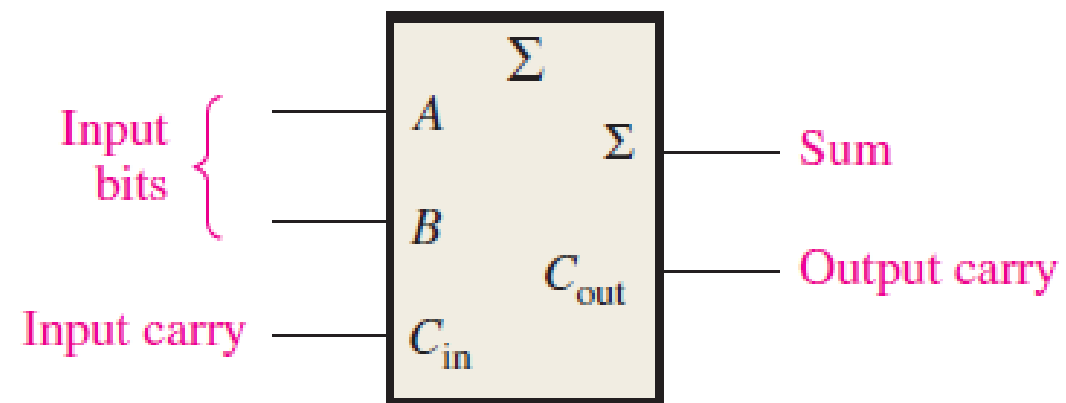

Block diagram of a Full-Adder


Half-Adder

- A half-adder accepts two binary digits on its inputs and produces two binary digits on its outputs- a sum bit and a carry bit.
- So a half-adder has two inputs and two outputs.
- Now to design a digital system we need to know its outputs for all the input combinations.
- The truth-table for the half adder can be constructed following the binary addition rule.
- The Boolean expression of the sum bit can be found as:

$$S = \bar{A}B + A\bar{B} = A \oplus B$$
- The Boolean expression of carry bit can be found as:

$$C_{IN} = AB$$
- So now a logical circuit can be drawn for a half-adder.

A	B	C _{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

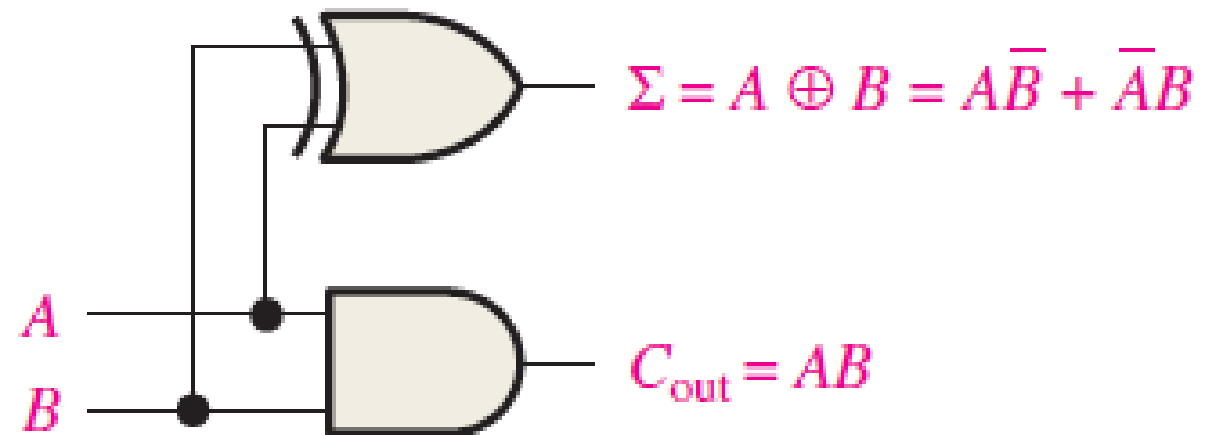

Full-Adder

- A full-adder accepts two input bits and an input carry and generates a sum output and a carry output.
- So a full adder has three inputs and two outputs.
- The truth table can be constructed the same way as we constructed for a half-adder.

A	B	C _{IN}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full-Adder


- After constructing the truth, now we can find the Boolean expressions

$$S = \bar{A}\bar{B}C_{IN} + \bar{A}B\bar{C}_{IN} + A\bar{B}\bar{C}_{IN} + ABC_{IN}$$

$$S = A \oplus B \oplus C$$

$$C_{OUT} = \bar{A}BC_{IN} + A\bar{B}C_{IN} + AB\bar{C}_{IN} + ABC_{IN}$$

$$C_{OUT} = AB + (A \oplus B)C_{IN}$$

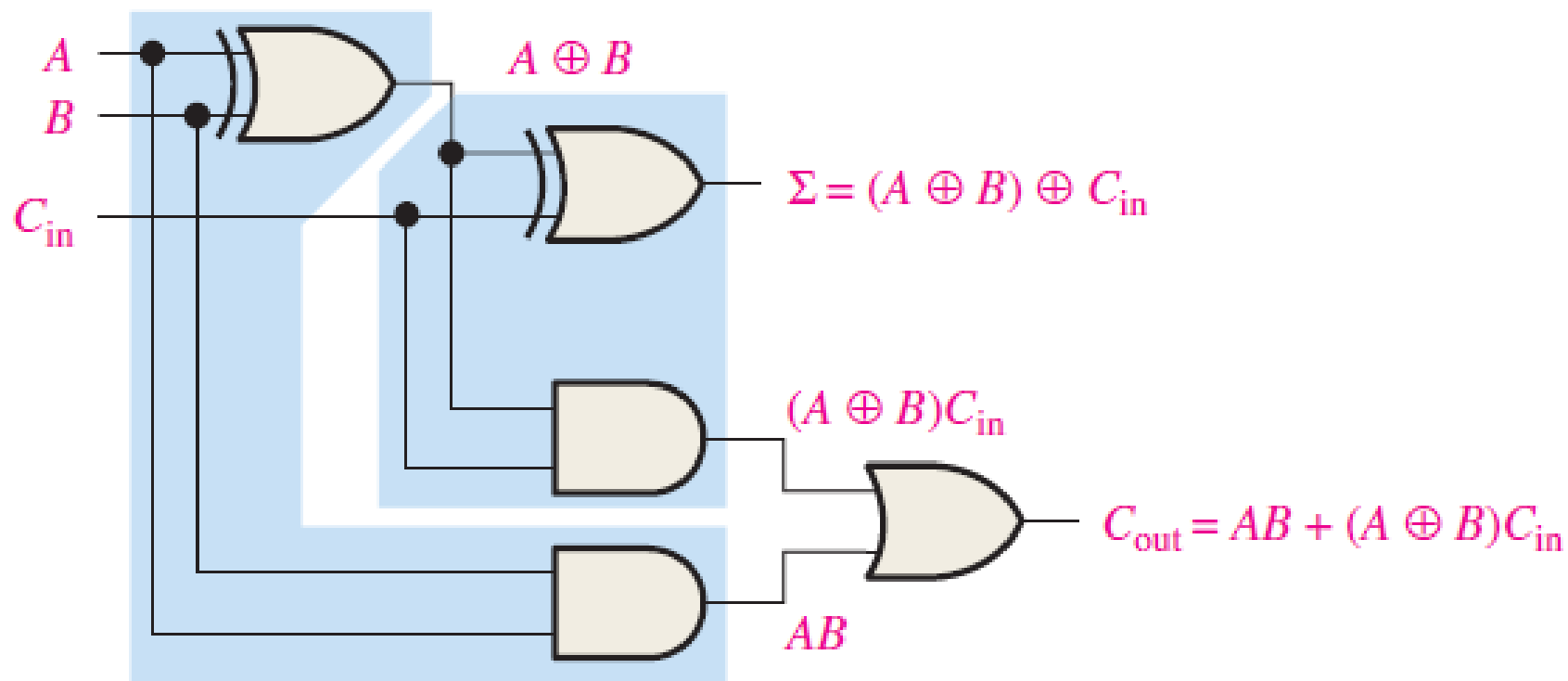


Parallel Adder

- Till now we have learned how add two numbers of 1 bit.
- So how do we add two number of two bits.
- The principle is same as we add two decimal numbers of two digits.
- We sum the first digits and below the first digits we write the sum and the generated carry is summed with the next digits.

Carry	1	
Number 1	2	9
Number 2	3	5
Sum	6	4


General format, addition of two 2-bit numbers:
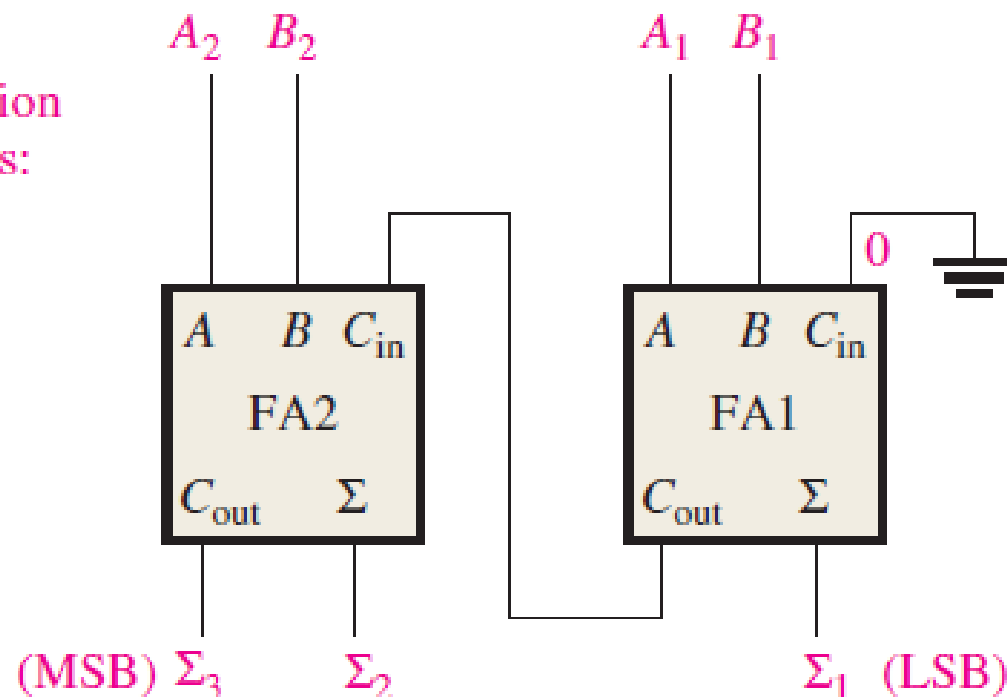
$$\begin{array}{r} A_2A_1 \\ + B_2B_1 \\ \hline \Sigma_3\Sigma_2\Sigma_1 \end{array}$$




Parallel Adder

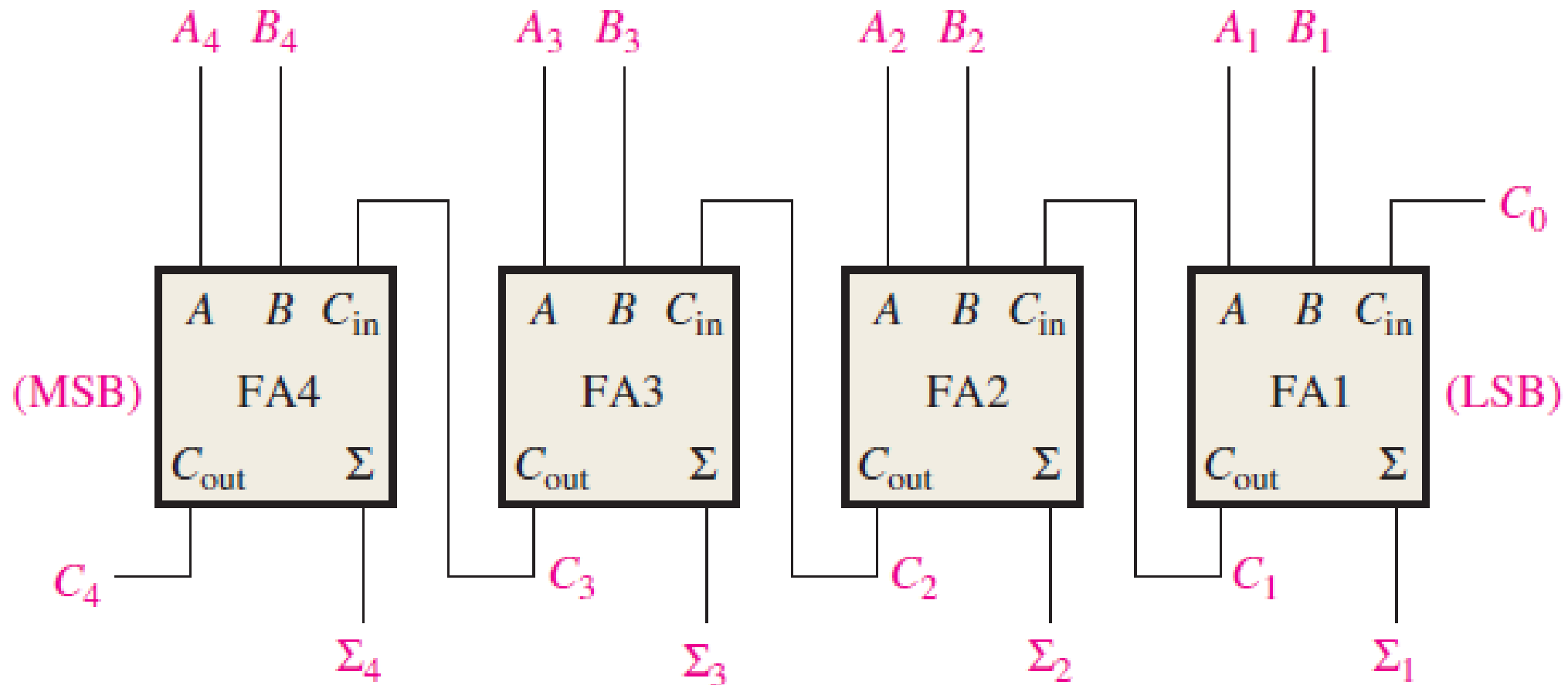- A 4-bit Parallel adder to add two 4bit numbers can be designed using the same principle.



Adder Expansion

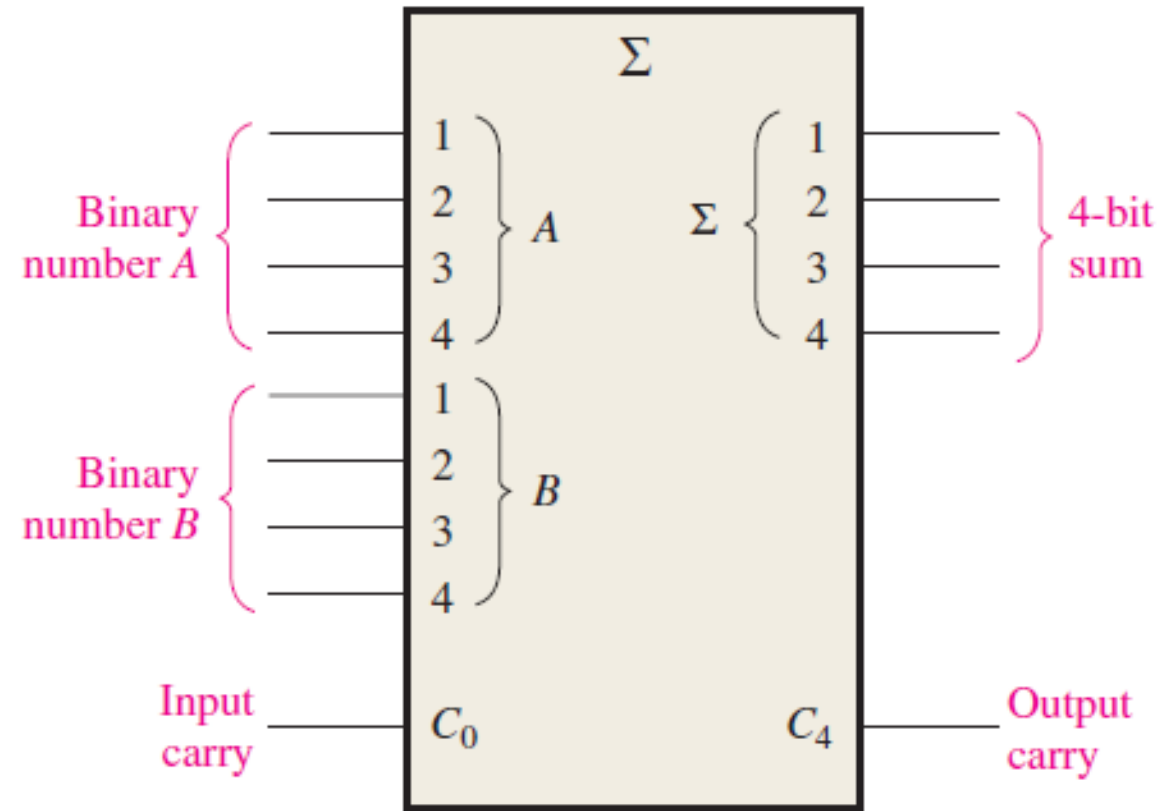
- We have learned how to add two 4-bit binary numbers.
- A 4-bit is called a nibble.
- So how do we add two numbers of 8-bits or even higher.
- That is when we use the concept of adder expansion.
- The following is the logic symbol used to represent a 4-bit parallel adder.




Adder Expansion

- We can cascade two blocks of 4-bit parallel adder to add two numbers of 8-bits.

		1	1	1					
	1	0	1	1		1	0	0	1
	1	0	0	1		1	1	1	0
1	0	1	0	1		0	1	1	1
C	S ₈	S ₇	S ₆	S ₅		S ₄	S ₃	S ₂	S ₁

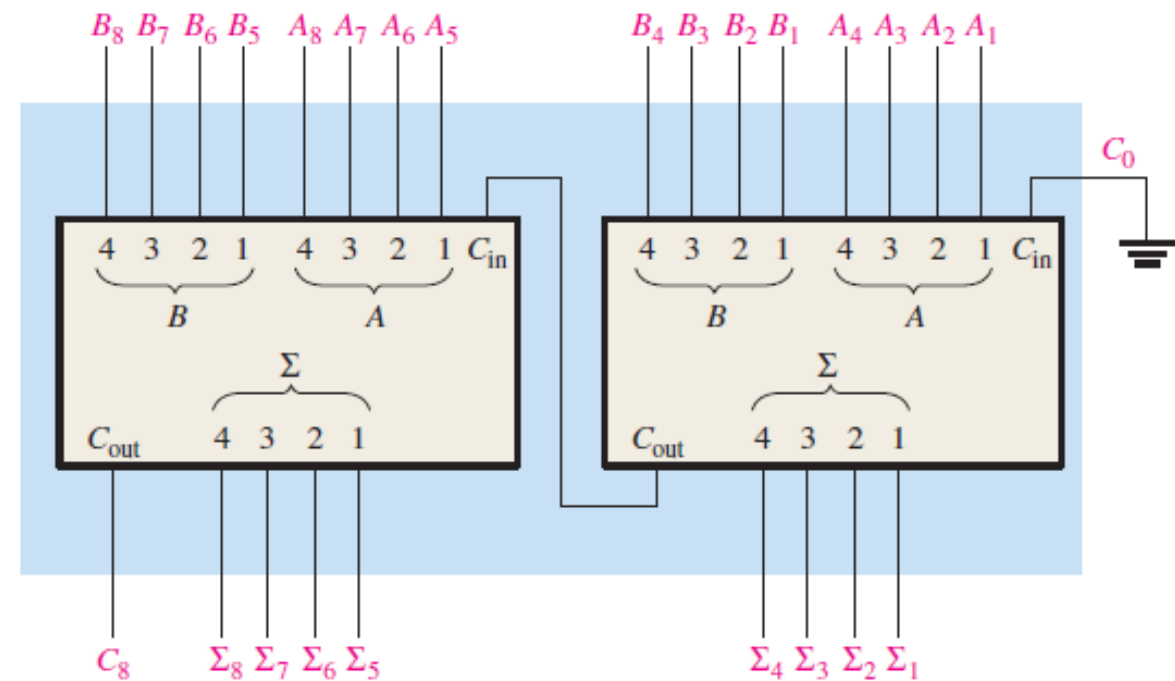

Example of Adder Expansion

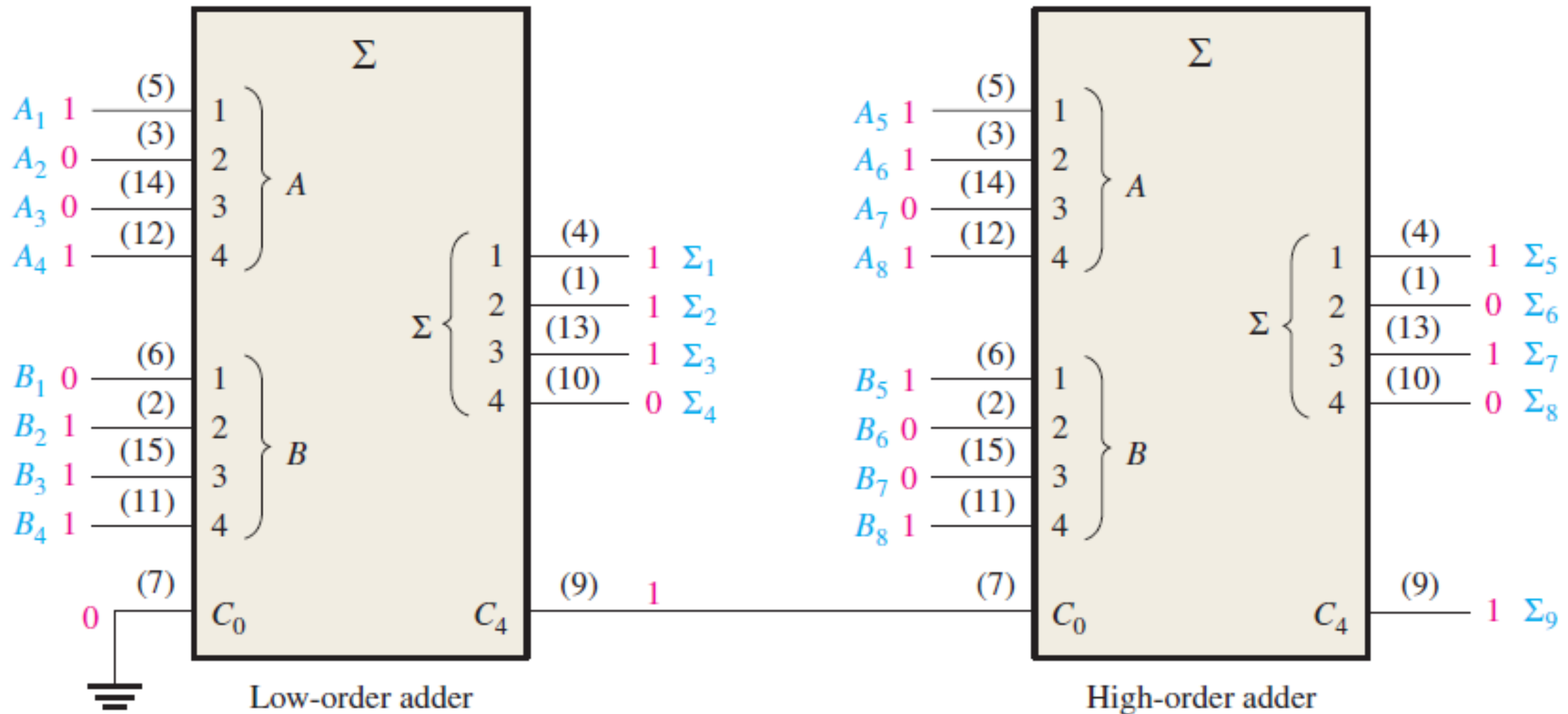

Subtractor

- A subtractor is a combinational circuit that take two numbers as input and produces their difference.
- It also has an output to specify if a 1 has been borrowed.
- The minuend is designated by **x** and the subtrahend is designated by **y**.
- Like adders, subtractors are also of two types namely, Half-subtractor and Full-subtractor.
- The rules of binary subtraction are:

X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0



Half-Subtractor

- A half-subtractor takes two binary bits as input and outputs the difference and borrow.
- The truth table for a half-subtractor is as follows:

X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0


$$D = \bar{X}Y + X\bar{Y} = X \oplus Y$$

$$B = \bar{X}Y$$

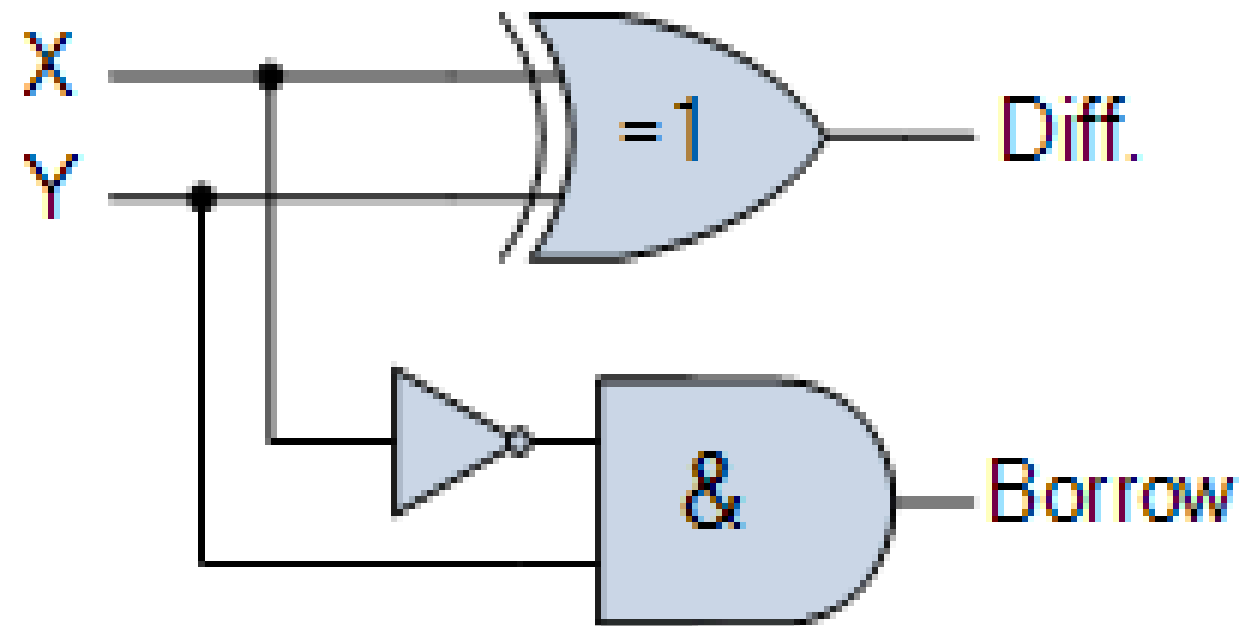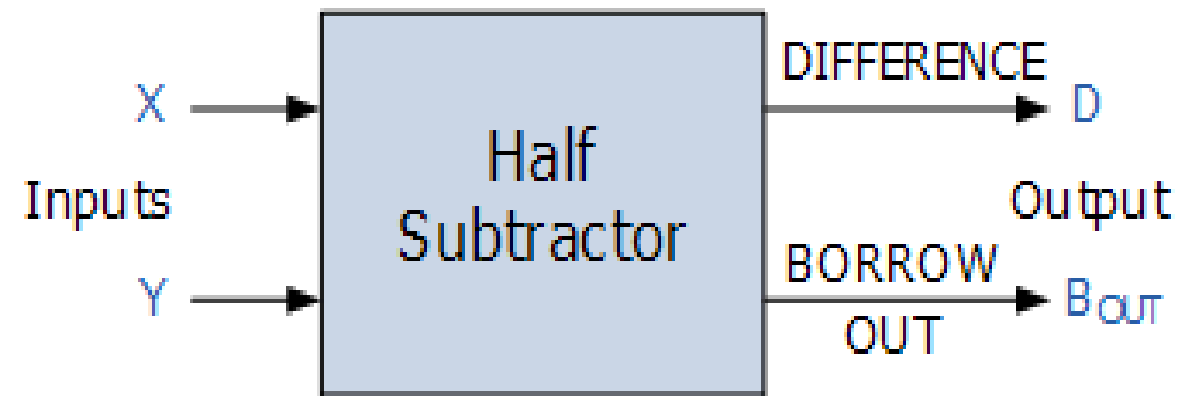

Full-Subtractor

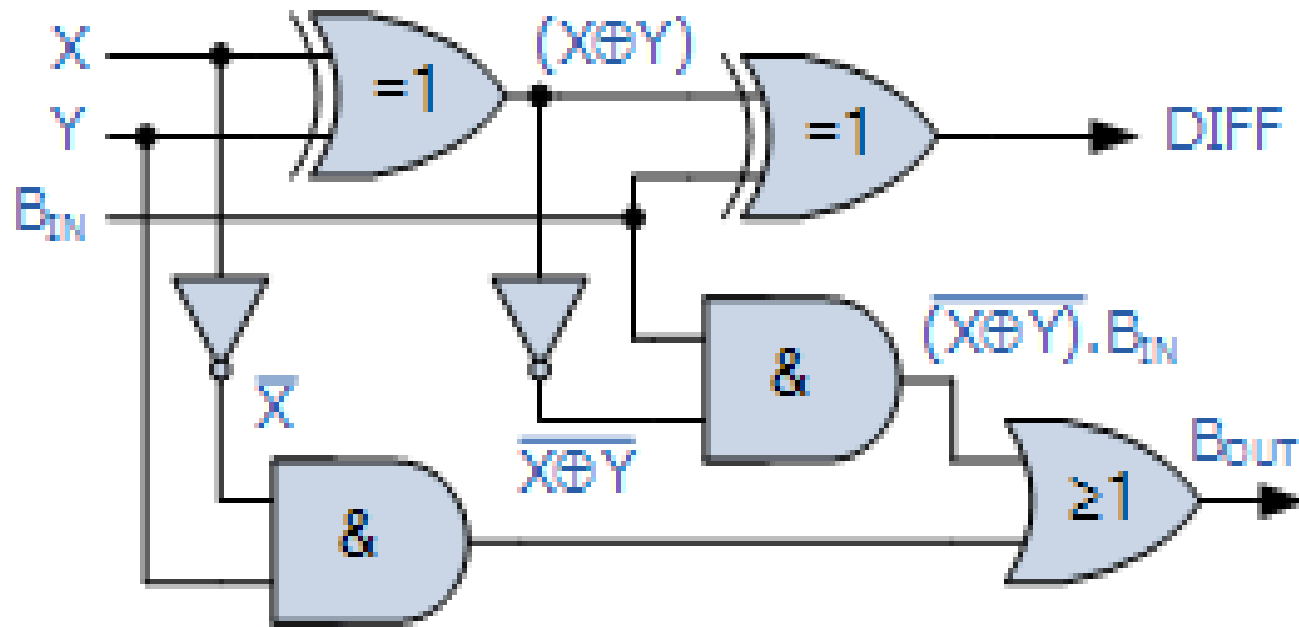- A full-subtractor takes the binary bits as input and outputs the difference and borrow.
- The truth table for a full-subtractor is as follows:




X	Y	B_{IN}	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = X \oplus Y \oplus B_{IN}$$

$$B = \bar{X}Y + \overline{(X \oplus Y)}B_{IN}$$

Digital Magnitude Comparator

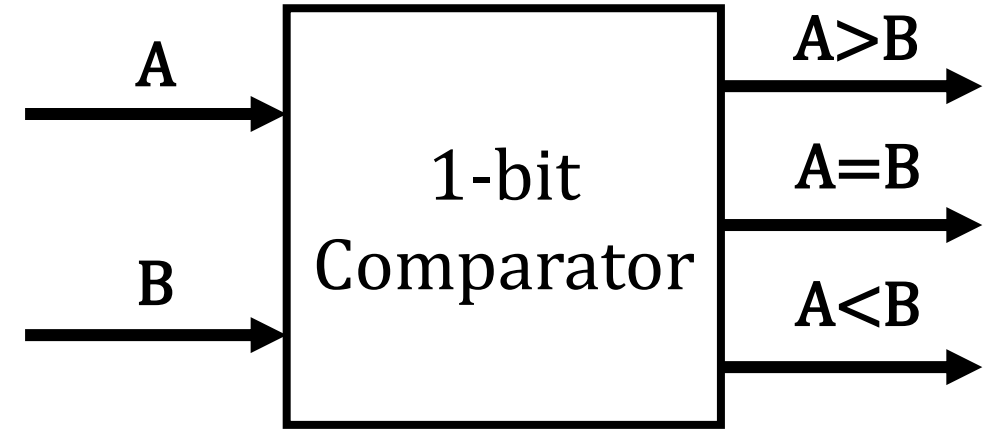- A comparator is a combinational circuit which can be used to compare between two number.
- A magnitude comparator has three possible outputs; A is greater than B, A is equal to B and A is less than B.
- The truth-table for a 1-bit comparator can be constructed as:



A	B	A>B	A=B	A<B
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

The Boolean expression for the outputs:

$$F_{A=B} = \bar{A}\bar{B} + AB$$

$$F_{A<B} = \bar{A}B$$

$$F_{A>B} = A\bar{B}$$



Digital Magnitude Comparator

The Boolean expression for the outputs:

$$F_{A=B} = \bar{A}\bar{B} + AB = \overline{A \oplus B}$$


$$F_{A<B} = \bar{A}B$$

$$F_{A>B} = A\bar{B}$$

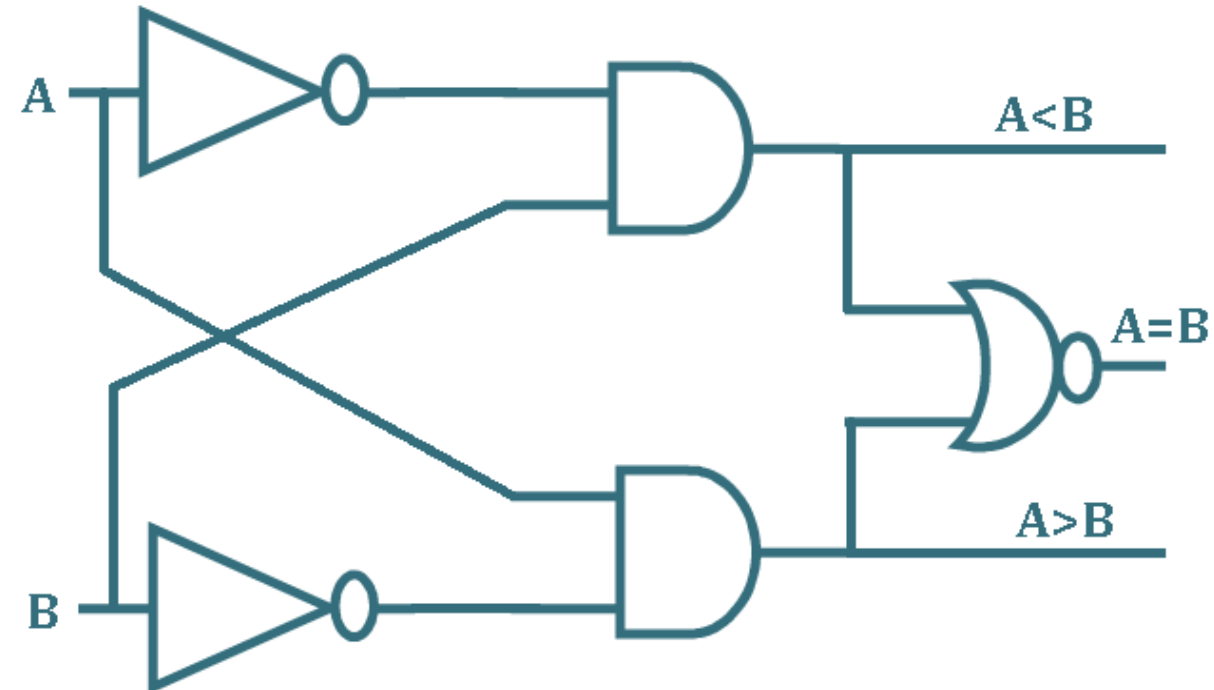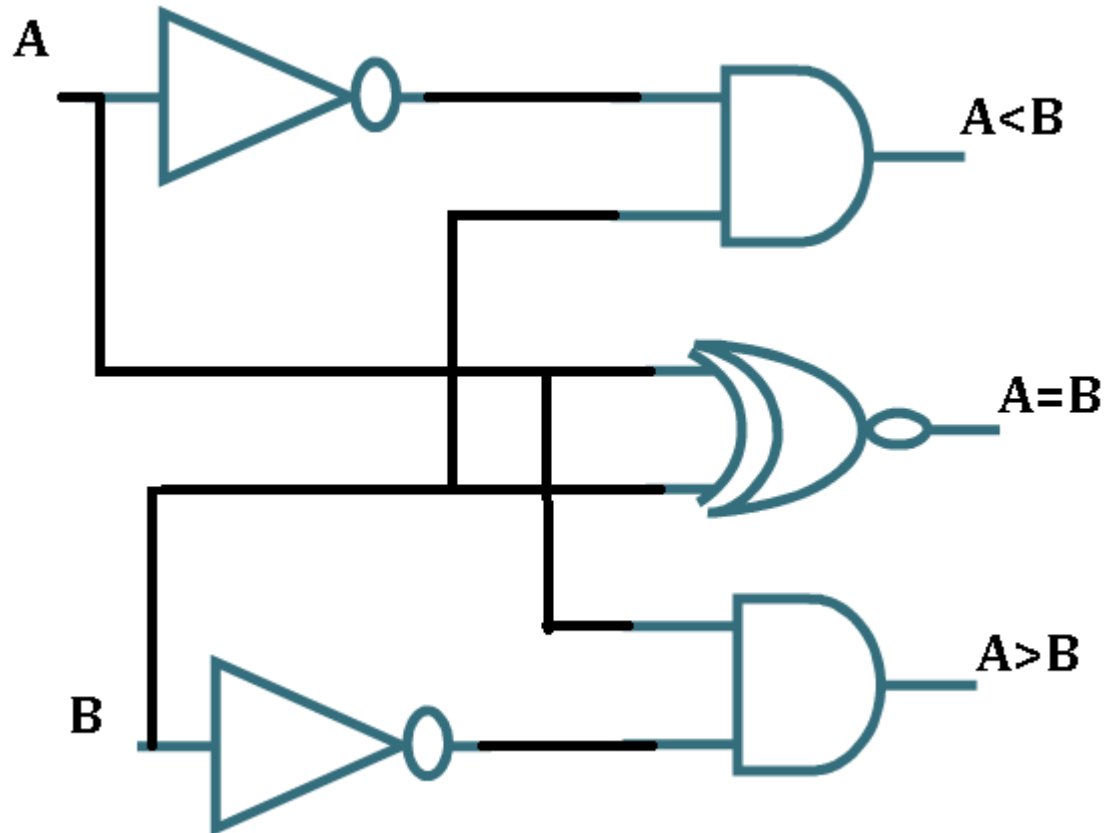

Digital Magnitude Comparator

- Two 1-bit comparators can be logically connected to make a 2-bit number comparator.
- The logic behind the connections are:
 - Let $X_0 = (A_0 == B_0)$ and $X_1 = (A_1 == B_1)$
 - For $A = B$, the Boolean expression is $X_1 X_0$
 - For $A > B$, the Boolean expression is $A_1 \overline{B_1} + X_1 (A_0 \overline{B_0})$
 - For $A < B$, the Boolean expression is $\overline{A_1} B_1 + X_1 (\overline{A_0} B_0)$

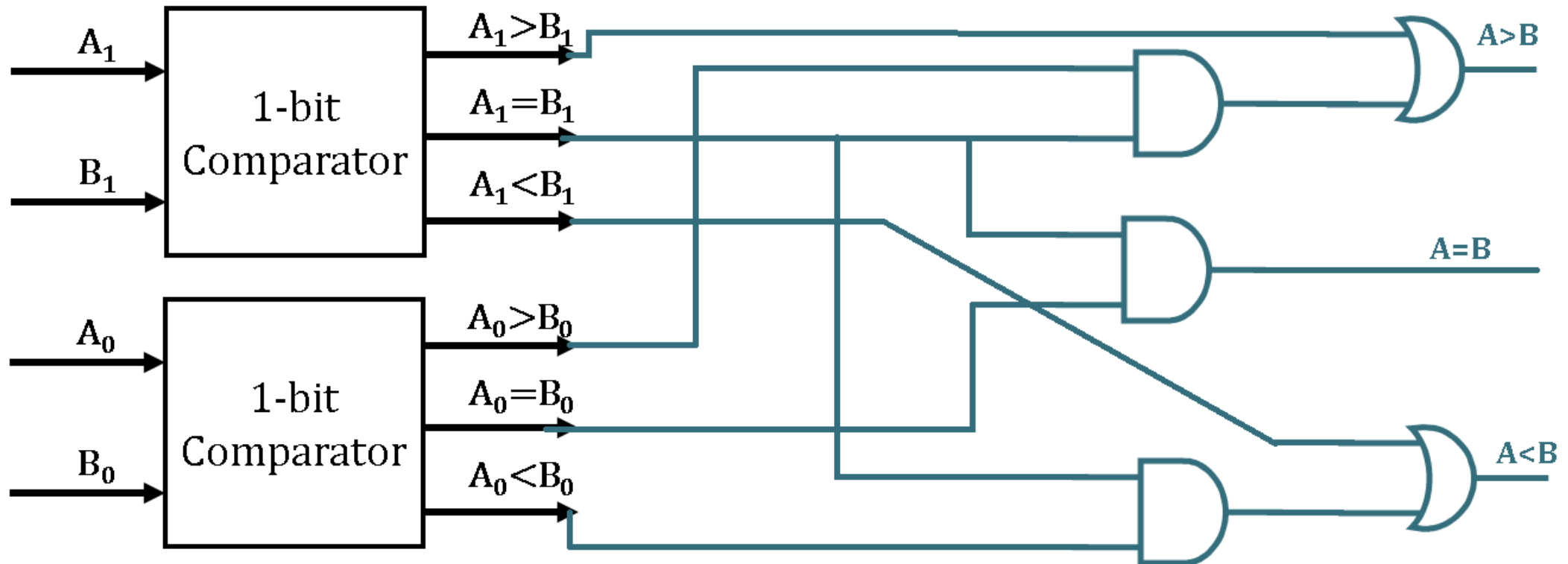

1. Thomas L. Floyd, “Digital Fundamentals” 11th edition, Prentice Hall – Pearson Education.

Thank You